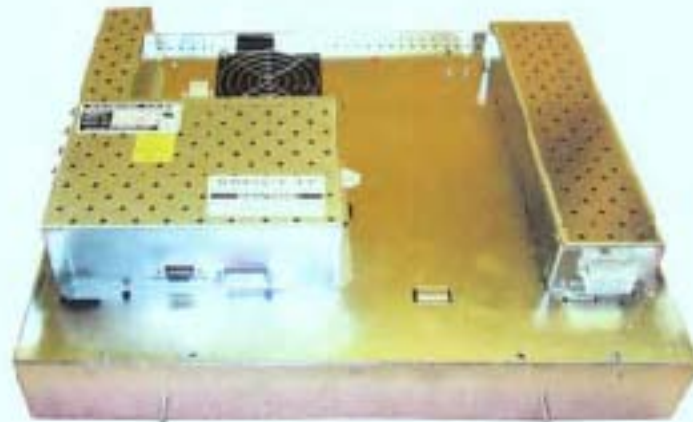


# Welcome

## *Amusement & Music Operators Association*


### **LCD Power Supply Troubleshooting Tech Seminar**



**INSTRUCTOR: Ray Holdren,**  
*Kokopelli Consulting LAS Vegas*  
*Instructor for CSN's Workforce Development Group*  
*Teacher for College of Southern Nevada, Cheyenne Campus, North Las Vegas, NV*


*Ray.Holdren@csn.edu*

## 11-Golden Rules of Safety

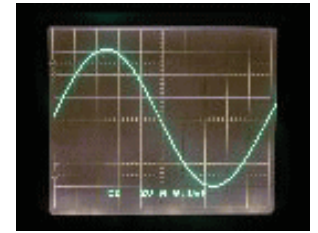


- 1. Anything with a AC plug must go into an isolation transformer.**
- 2. Remove all jewelry ( rings,watches,chains, hanging I.D. Cards) when working on anything electrical or electronic.**
- 3. Always hook instrument *ground* (Black) connection up first.**
- 4. Only one hand touching chassis or circuit components; preferably right hand; with fingers pointing up.**
- 5. *Never* place one hand on one piece of electronic equipment then one hand on a separate piece of electronic equipment.**
- 6. Always use Safety Ground Strap when working the Bench or on site.**

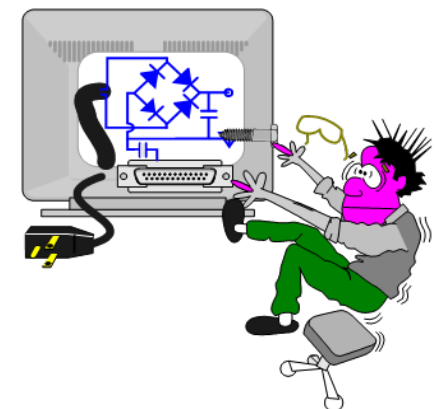- 7. When working with an Electronic Trainer with Trouble Switches, turn power to Trainer off, switch in Trouble Switch, turn Trainer on.**
- 8. Electronics and liquids do not mix. (no drinks on working benches please)**
- 9. Use *all* senses *all* the time. See, hear, feel, smell or sense something not right, power down Bench or product under test.**
- 10. Power Down Bench when leaving for any period of time.  
(preferably with one Bench Master Power Switch)**
- 11. Don't Feel Well? Take a Break or Go Home!**




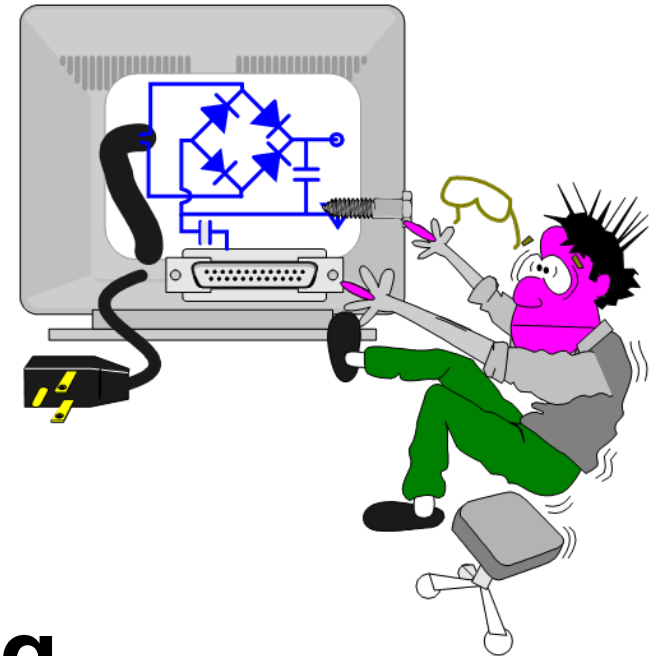- ✓ **Use an Isolation Transformer!**
- ✓ **Remove power first!**
- ✓ **Read each procedure carefully!**
- ✓ **Use common sense!**
- ✓ **Take precautions working around and handling CRTs!**
- ✓ **Ask for help!**



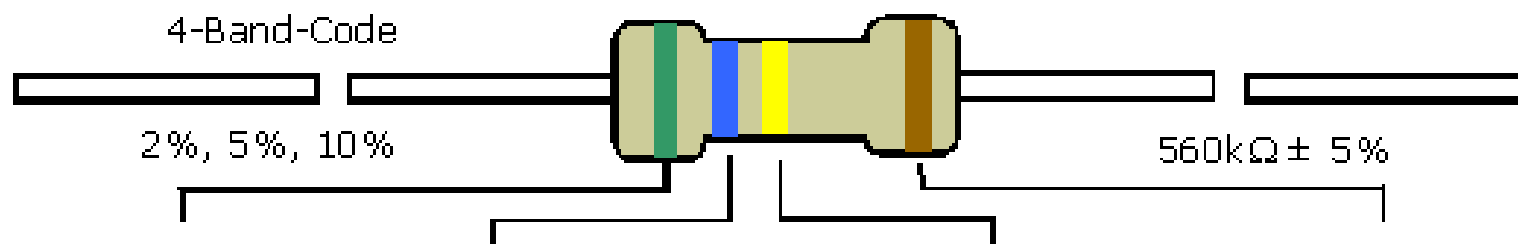
# CRT Handling Dangers

- **CRTs are constructed with a near-perfect vacuum**  
Implosion risk
- **CRTs operate at high voltages up to 30kV (30,000 volts)**
- **Be careful when chassis is running**  
shock (HV won't kill you but your reaction might)  
arcing will damage components
- **Be careful when chassis is off**  
CRTs rebuild charge after being discharged



COLOR	1st BAND	2nd BAND	3rd BAND	MULTIPLIER	TOLERANCE	
Black	0	0	0	1 $\Omega$		
Brown	1	1	1	10 $\Omega$	$\pm$ 1%	(F)
Red	2	2	2	100 $\Omega$	$\pm$ 2%	(G)
Orange	3	3	3	1K $\Omega$		
Yellow	4	4	4	10K $\Omega$		
Green	5	5	5	100K $\Omega$	$\pm$ 0.5%	(D)
Blue	6	6	6	1M $\Omega$	$\pm$ 0.25%	(C)
Violet	7	7	7	10M $\Omega$	$\pm$ 0.10%	(B)
Grey	8	8	8		$\pm$ 0.05%	
White	9	9	9			
Gold				0.1	$\pm$ 5%	(J)
Silver				0.01	$\pm$ 10%	(K)

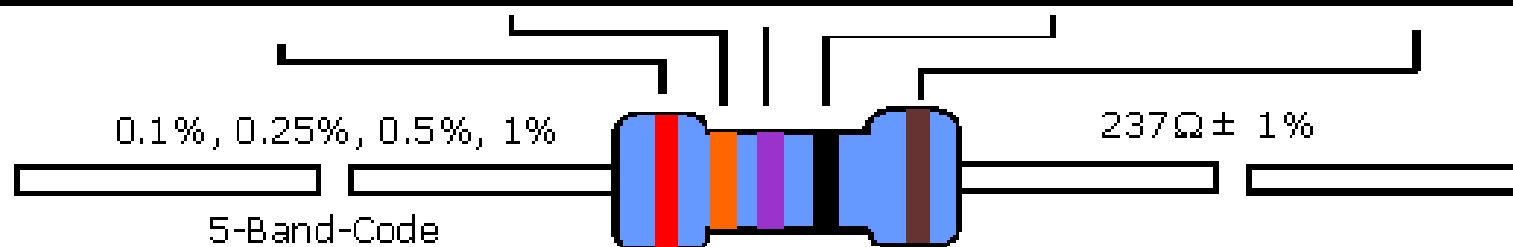

## Oscilloscope Operation Tips

- **Select correct CRT MODE**
  - CH A, CH B, CH A&B
- **Use AC input coupling**
- **Set timebase (TIME/DIV) to match signal**
  - 2mS - 5mS for low frequency waveforms
  - 2 $\mu$ S - 10 $\mu$  S for high frequency waveforms
- **Set vertical sensitivity (VOLTS/DIV) to match signal level**
  - use digital VPP meter as guide
- **Set Horizontal & Vertical position controls**
- **Set trigger source to the channel being used (A or B)**
- **Set TRIGGER MODE to the AUTO position**
- **Adjust TRIGGER LEVEL until a stable waveform is displayed**

***And now:***

***Reference TS400 Book***

## Switch Mode Power Supplies

- **Power Supply Theory of Operation**
  - Power Supply Basics
  - Safety Concerns
  - Common Switch Mode Power Supply (SPMS) Types
  - Functional Block Diagram
- **Pulse Width Modulation (PWM) SMPS Familiarization**
- **Hands-On PWM SMPS Troubleshooting**
- **Pulse Rate Modulation (PRM) SMPS Familiarization**
- **Hands-On PRM SMPS Troubleshooting**
- **Component Analyzing**
- **Review**

**All electronic systems require a power supply**

**Focus on two common switching power supplies**

- ◆ **Pulse Width Modulated (PWM)**
- ◆ **Pulse Rate Modulated (PRM)**


**These supplies utilize AC line derived DC supplies**

- ◆ **Raw B+ supply**

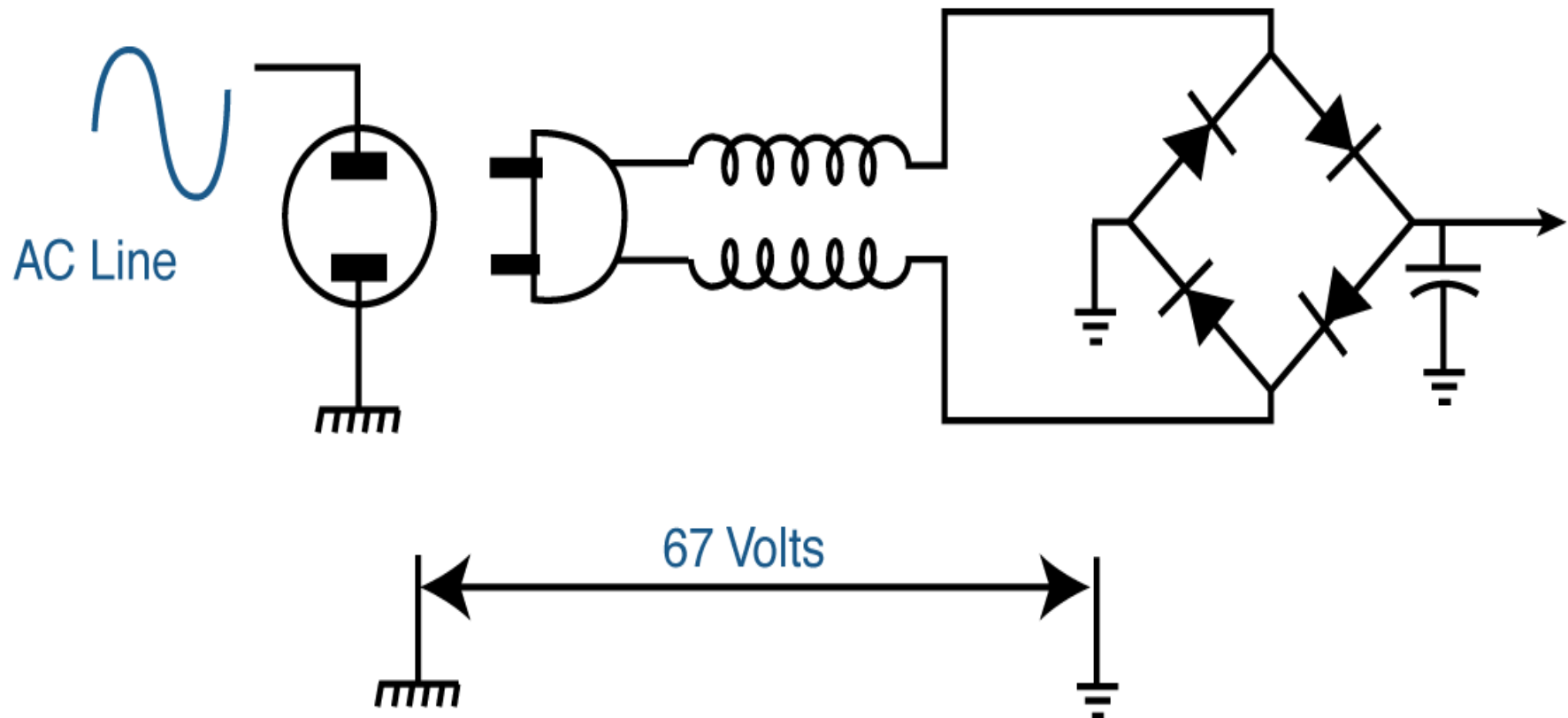**Two common Raw B+ supplies**


- ◆ **Half-Wave Rectifier**
- ◆ **Full-Wave Bridge Rectifier**

- Full-Wave Bridge Rectifier & Filter
- Commonly used to provide SMPS raw B+






## Half-Wave AC Rectifier & Filter


- low power application

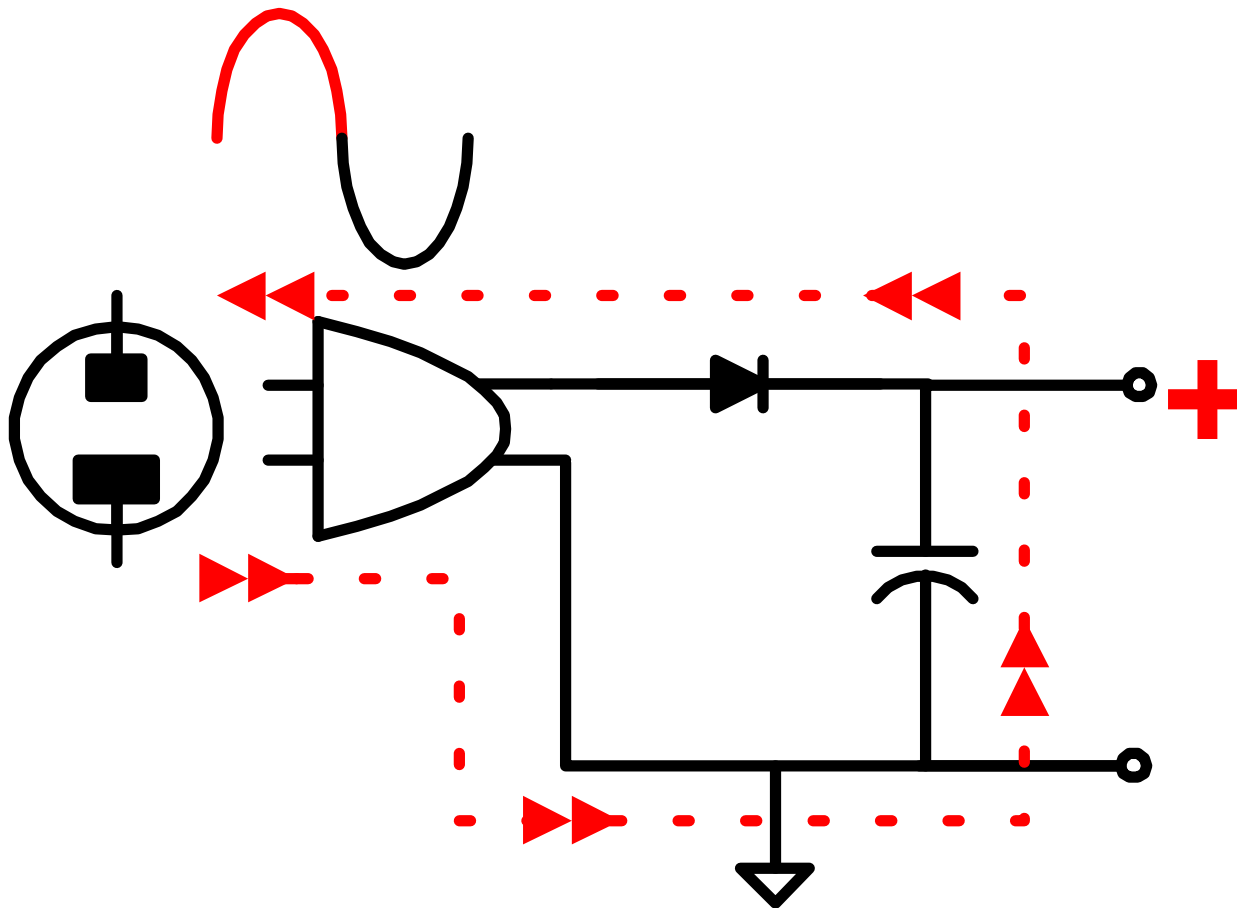


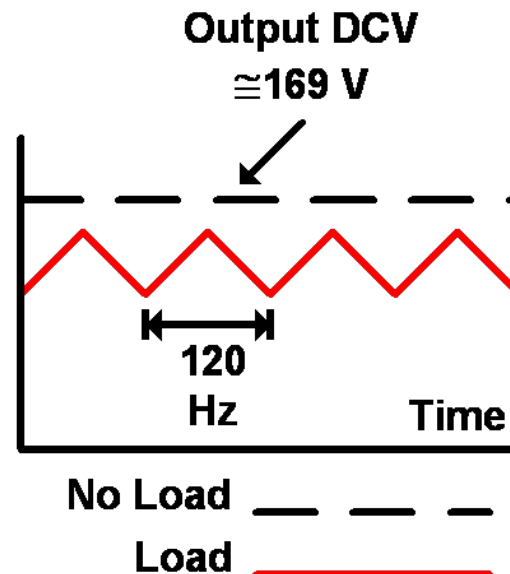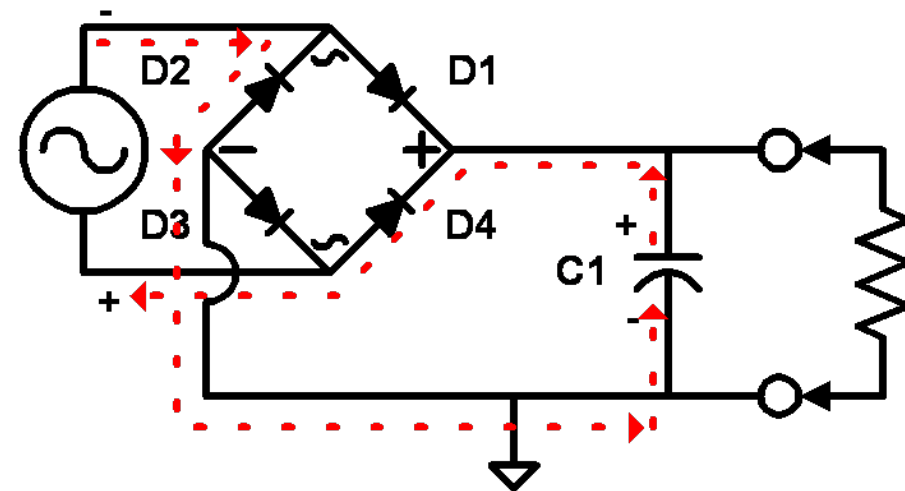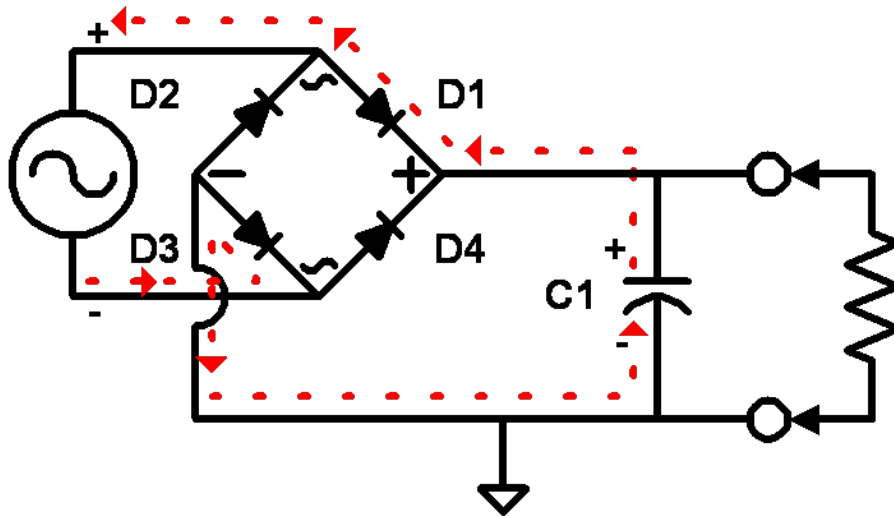Each half cycle of the 60Hz AC input voltage turns on different diodes in the bridge rectifier



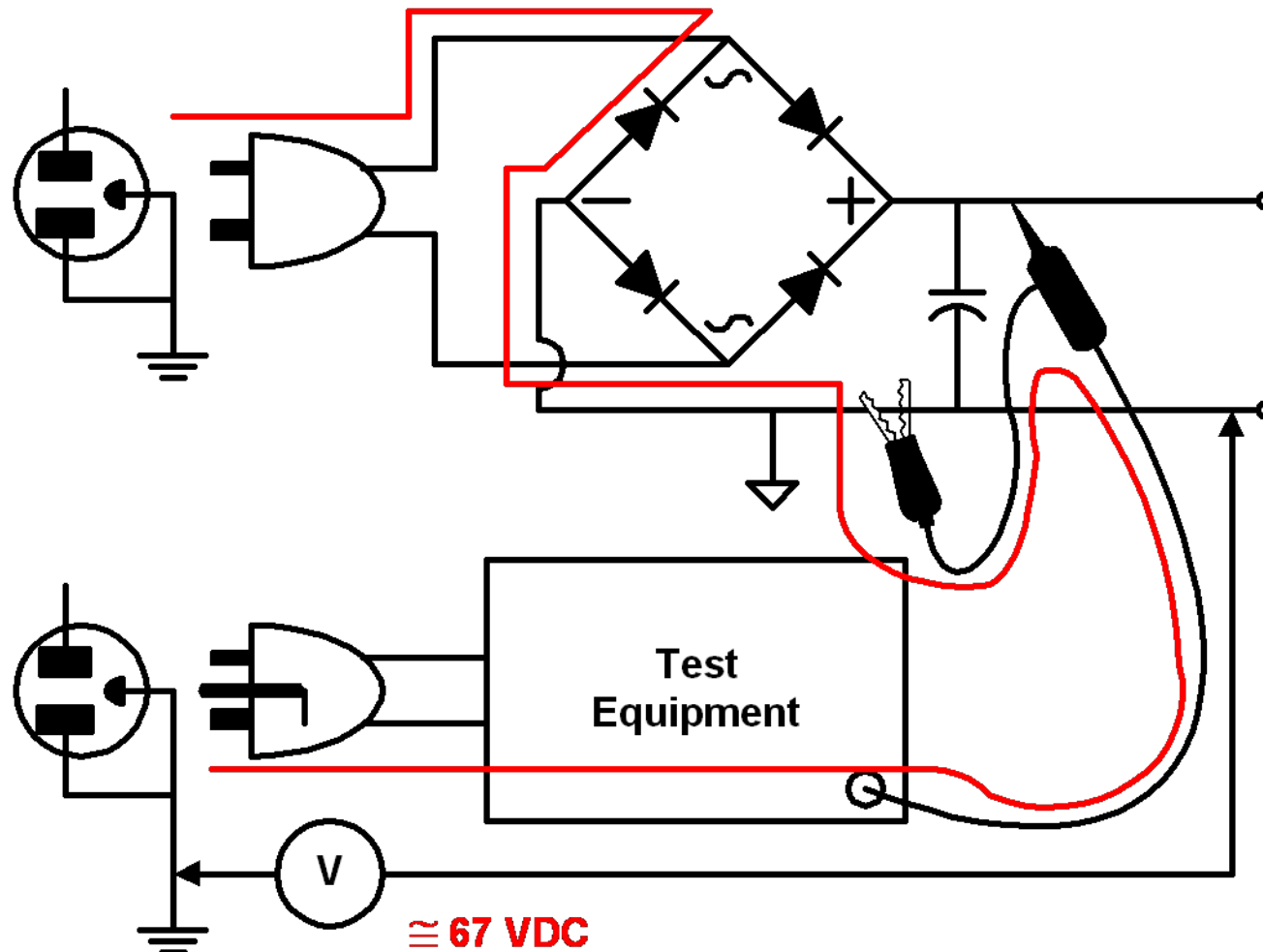- Full wave supplies are **ALWAYS** hot ground
- *Damage to Test Equipment and to the monitor can occur!*



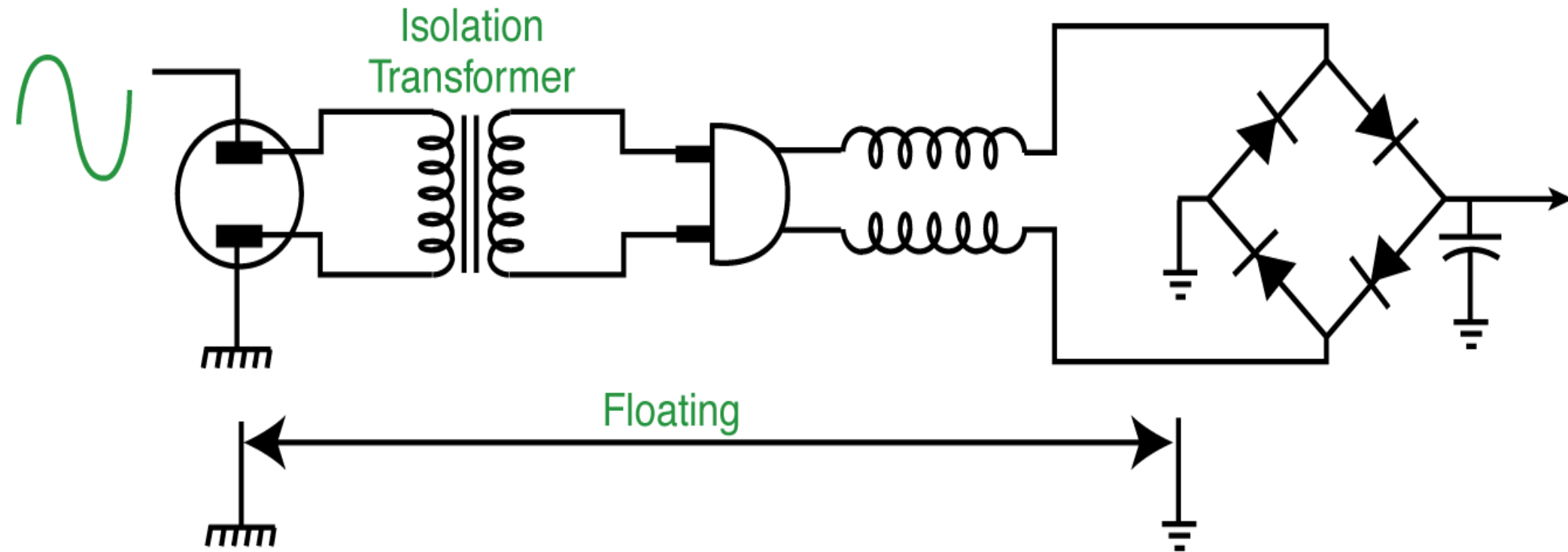

- Isolation transformer breaks DC electrical connection
- Allows chassis to float to earth ground potential
- Safe to connect the ground of oscilloscope

1. **ALWAYS** plug the **monitor** into an isolation transformer.
2. **Never connect test equipment to the isolation transformer.**
3. **Do not defeat the 3rd wire safety ground.**
4. **Connect only one monitor at a time to the isolation transformer.**

### What Is AC Leakage?


- ◆ Any current path that develops to what is normally an insulated part
- ◆ Any path which places the user in direct or indirect contact with the AC line

### What Causes AC Leakage?

- ◆ Defective AC line or switching supply isolation transformer
- ◆ AC bypass capacitors
- ◆ Improper parts installation
- ◆ Foreign objects
- ◆ Improper case and mounting screws

# AC Safety Leakage - Effects


# Servicing Safety

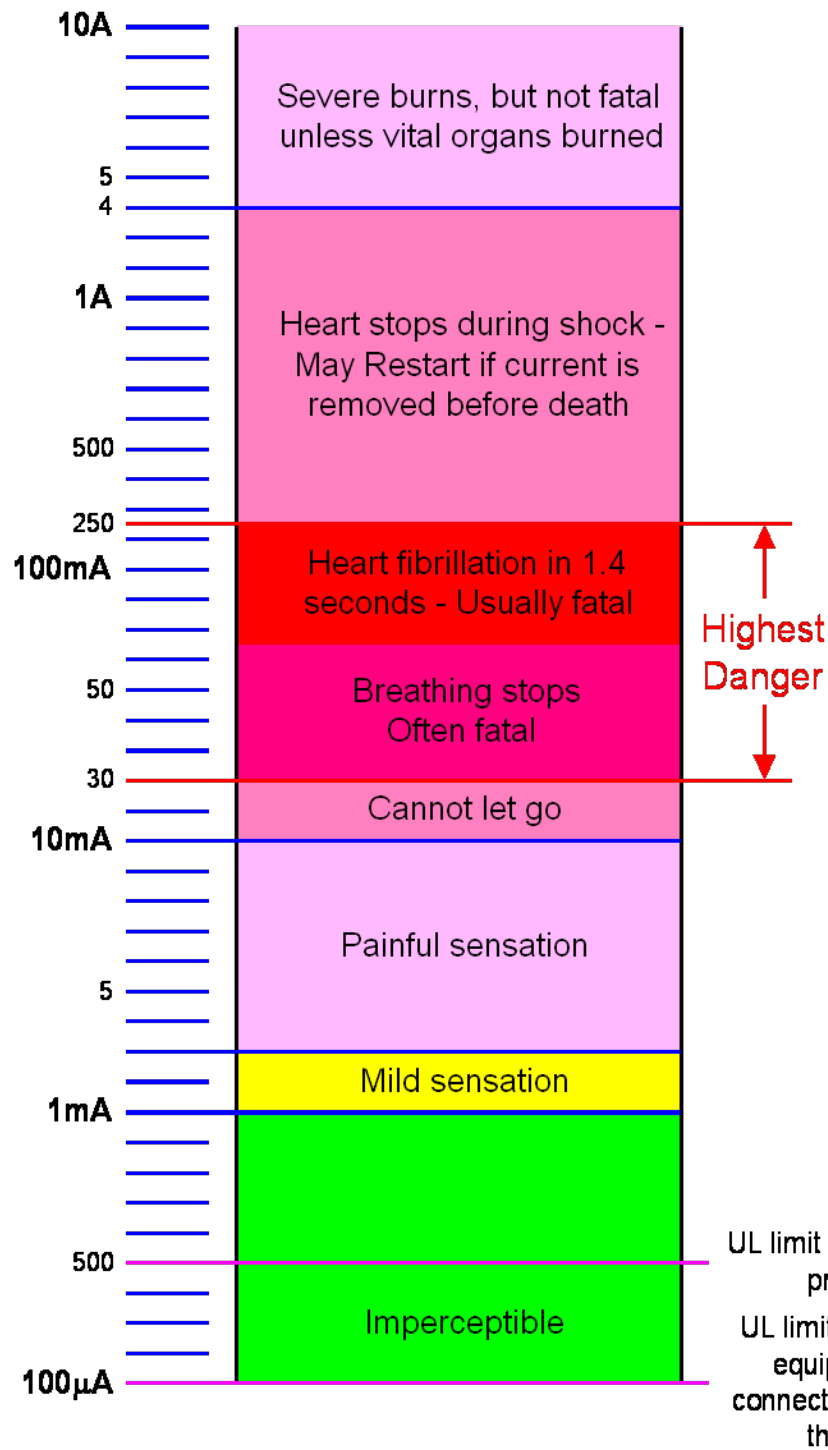


- **Safety leakage test ensures that monitor doesn't have AC leakage to exposed metal parts**
- **Service literature specifies that a safety leakage test be performed at the completion of all repairs**
- **Safety leakage testing applies to all consumer electronic devices powered from the AC line, whether or not they have a 3-wire power cord**
- **Underwriter's Laboratory (UL) standard is 500 ma**
- **Other standards may apply**
- **International Electrotechnical Commission (IEC) standard is 700  $\mu$ a**

# Typical Safety Leakage Test

## Servicing Safety

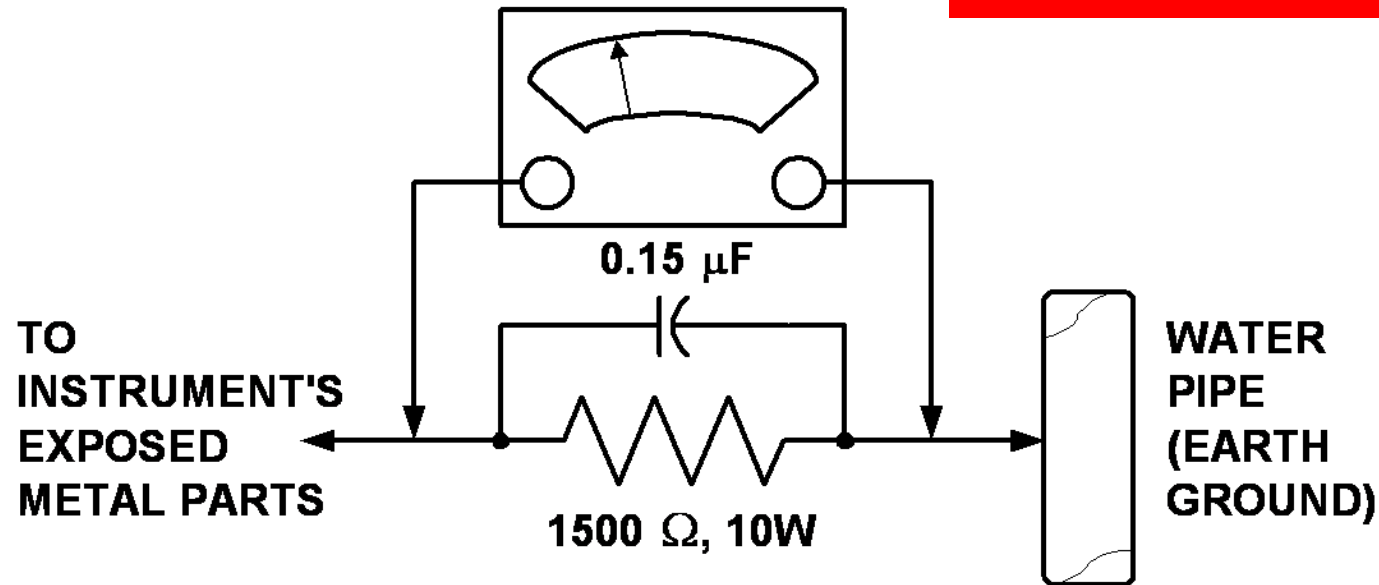


- 1 Do not use an isolation transformer for this test. Plug the completely reassembled unit directly into the ac outlet.
- 2 Connect a 1.5K, 10W resistor paralleled by an .015uF capacitor between each exposed metal cabinet part and a good earth ground such as a water pipe, as shown above.
- 3 Use an ac voltmeter with at least 5000 ohms/volt sensitivity to measure the potential across the resistor.
- 4 The potential at any point should not exceed 0.75 volts. A leakage current tester may be used to make this test; leakage current must not exceed 0.5 milliamps. If a measurement is outside of the specified limits, there is a possibility of shock hazard. The chassis should be repaired and rechecked before returning it to the customer.
- 5 Repeat the above procedure with the ac plug reversed. (Note: An ac adapter is necessary when a polarized plug is used. Do not defeat the polarizing feature of the plug.)

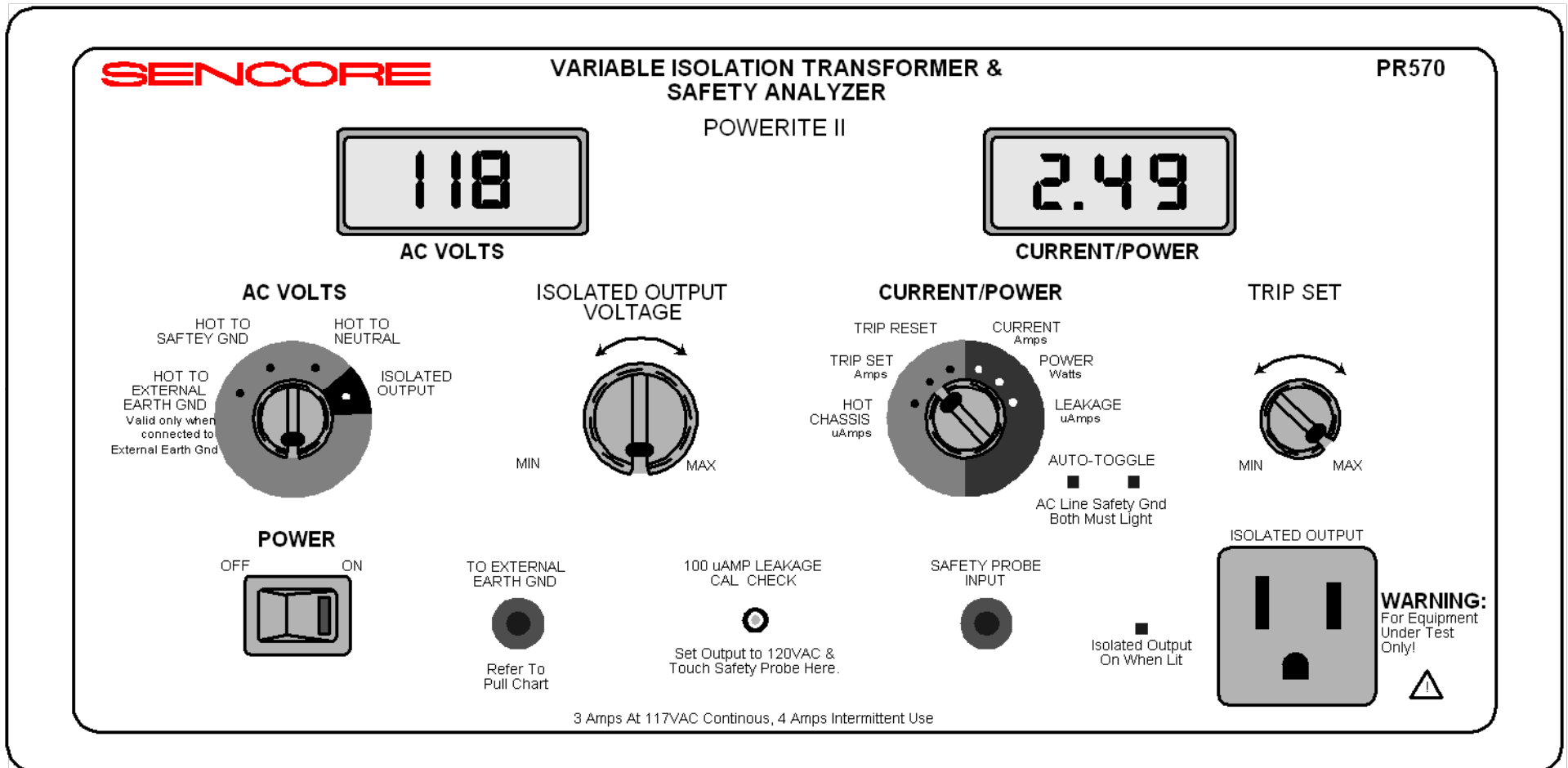

◆ Variable Isolation Transformer

◆ Safety Analyzer

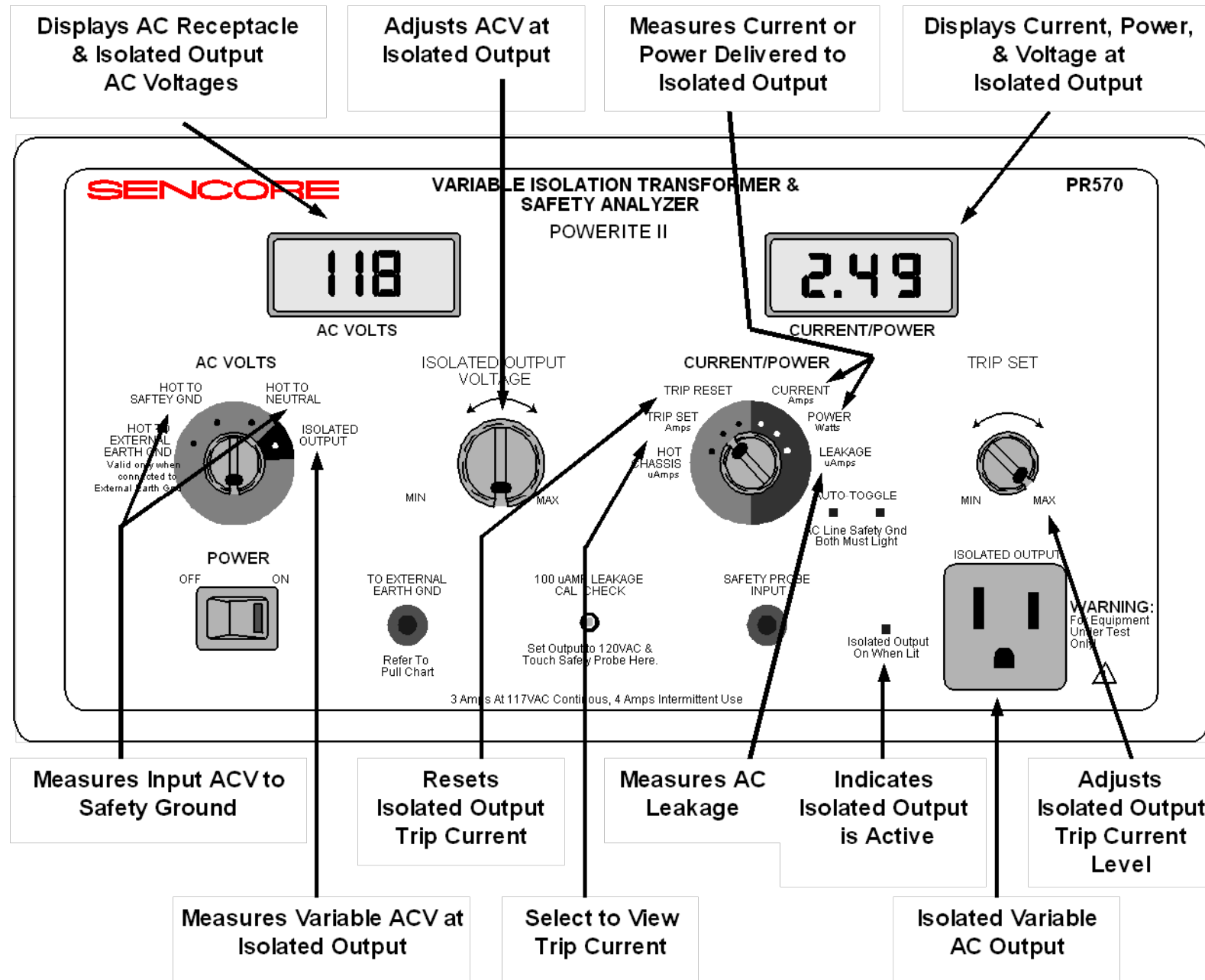

- ◆ **Raw B+ power supply has only one output and no regulation**
- ◆ **Power supplies must maintain a constant output voltage**
  - ◆ **Must detect and compensate for AC line voltage variations and load changes**
- ◆ **Three ways to regulate power supply output voltages:**
  - ◆ **Series Linear Pass**
  - ◆ **PWM Switch Mode Power Supply**
  - ◆ **PRM Switch Mode Power Supply**


## ◆ SMPS advantages vs. linear supply

- ◆ Higher efficiency
- ◆ Tighter output voltage regulation
- ◆ Smaller size and weight

## ◆ Early SMPS

- ◆ Mechanical vibrator used in early automobiles
- ◆ TV and monitor scan derived power supplies
- ◆ SMPS troubleshooting can be confusing, costly & frustrating without a logical and controlled troubleshooting procedure

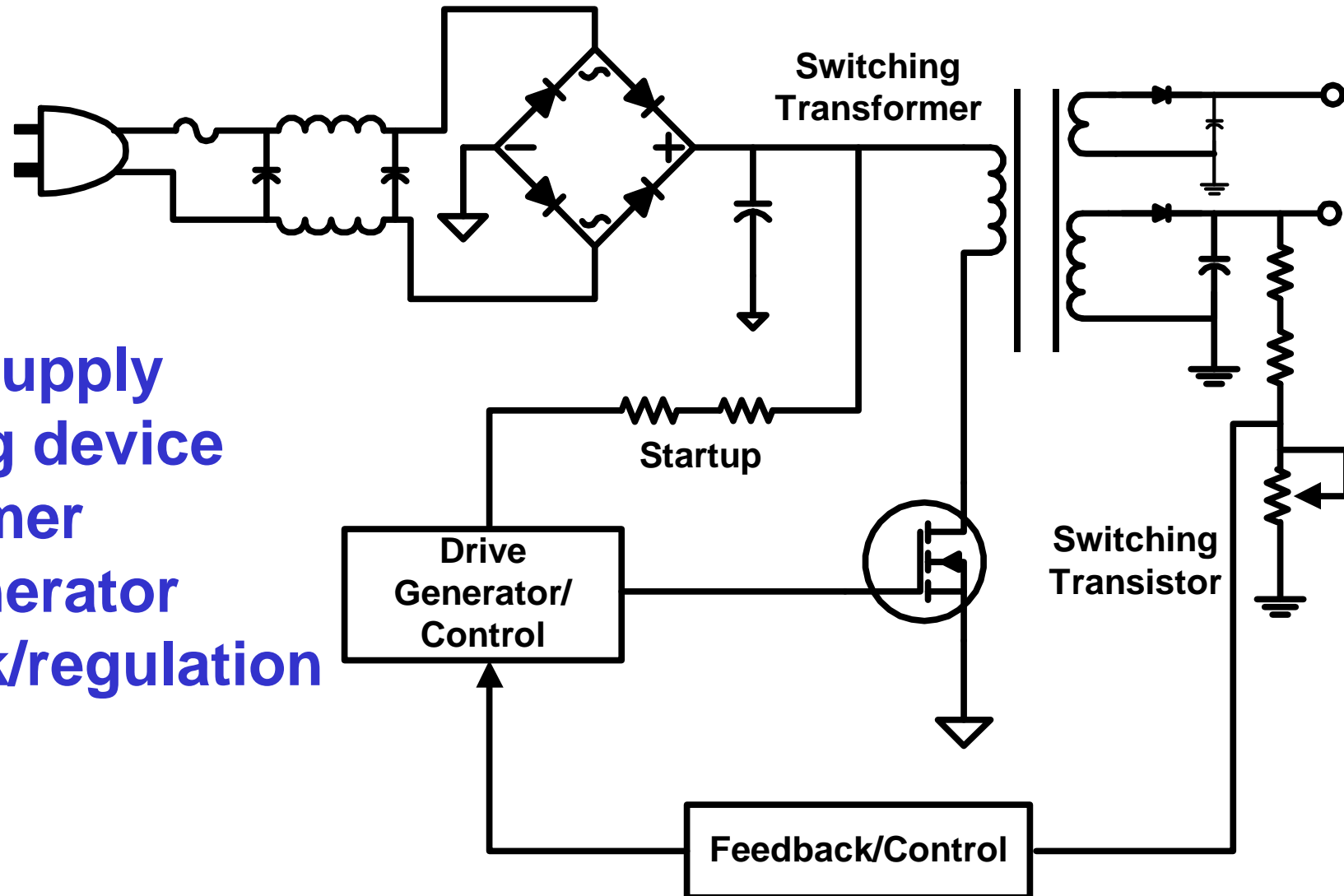**All SMPs include these basic operational blocks:**




- Raw B+ supply
- Switching device
- Transformer
- Drive generator
- Feedback/regulation
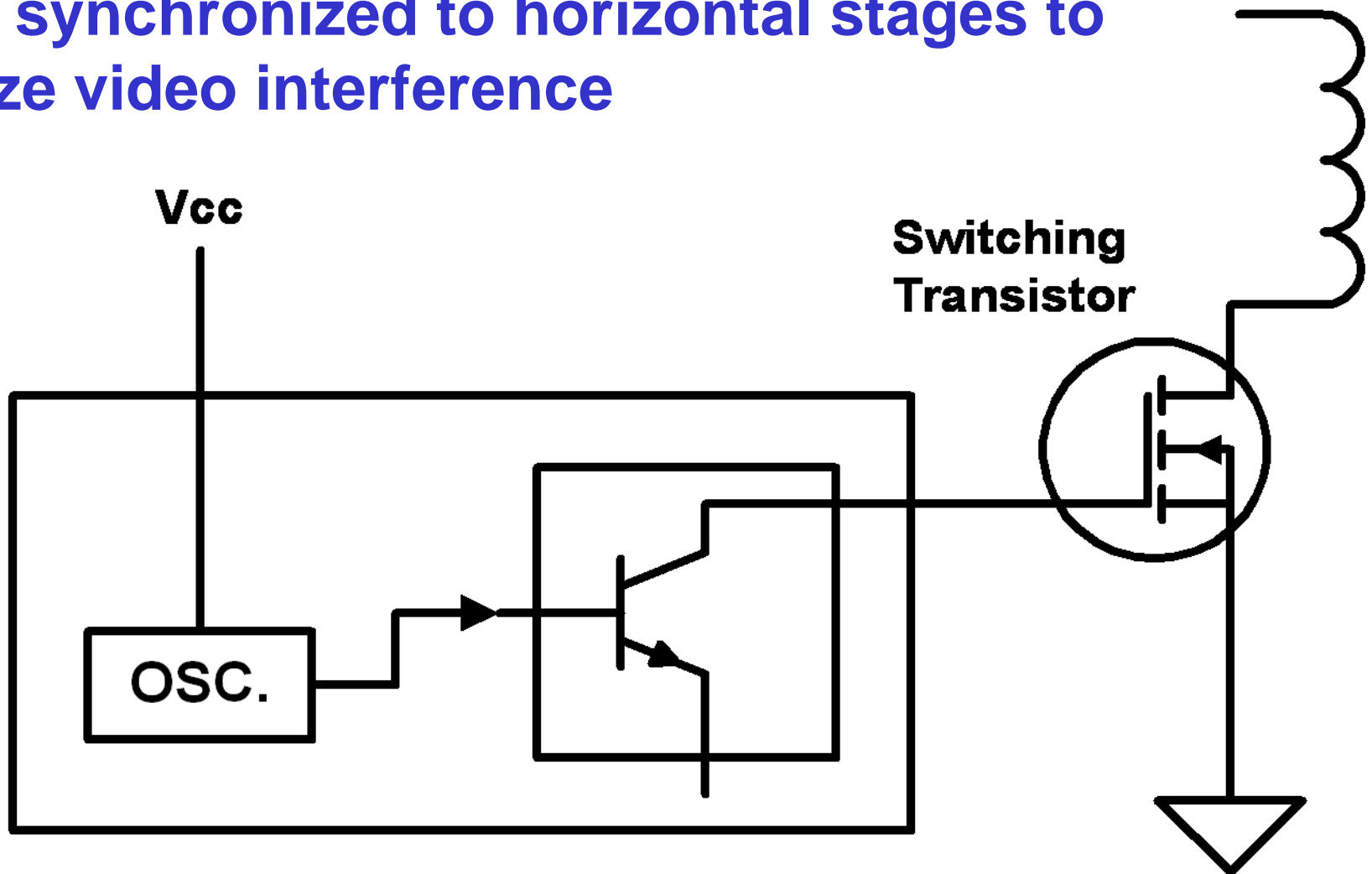
### Pulse Width Switching Supply


Drive = IC Oscillator

Can be synchronized to horizontal stages to minimize video interference




### Pulse Rate Switching Supply


Drive = Self-Oscillation

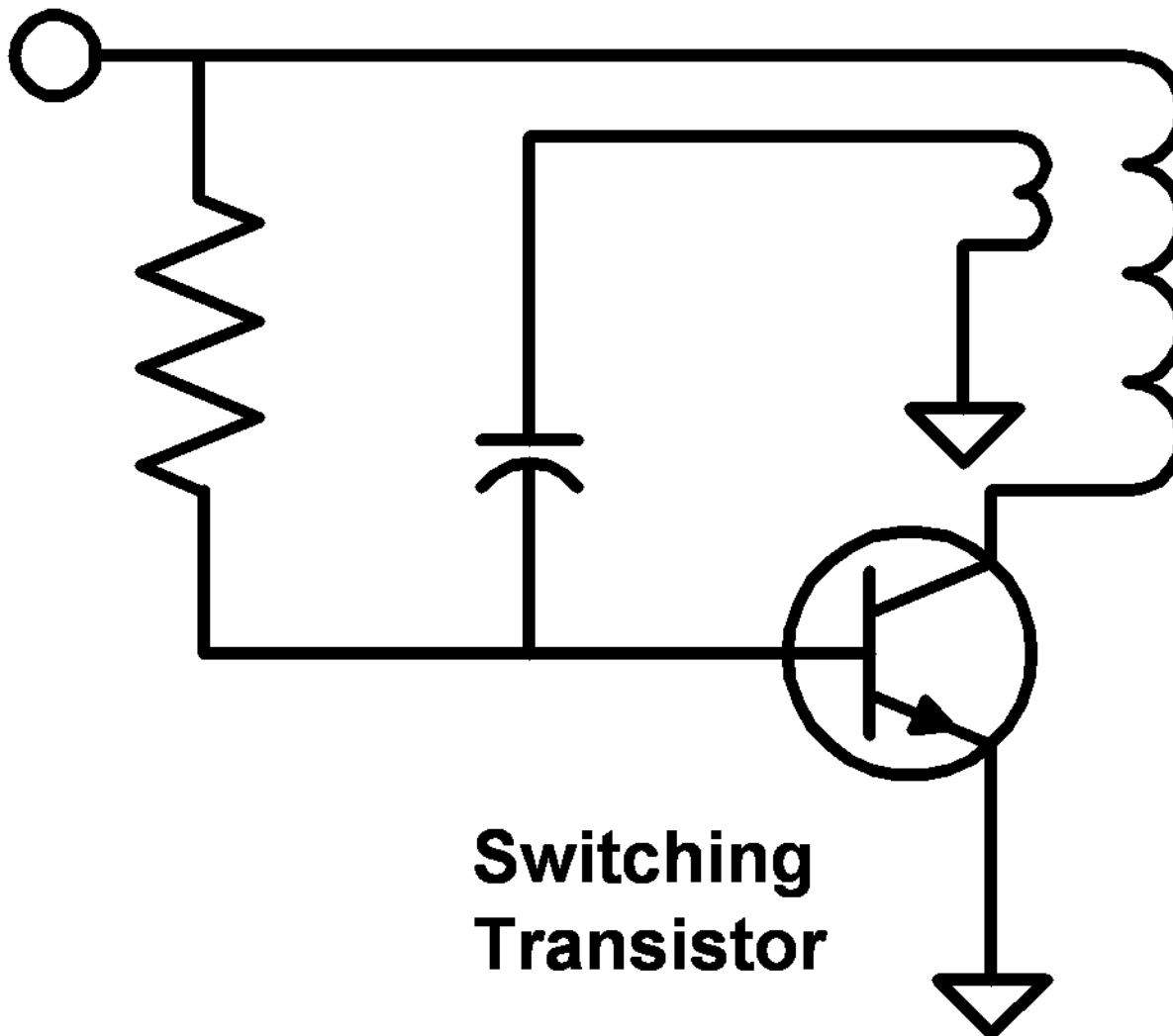

### Pulse Width

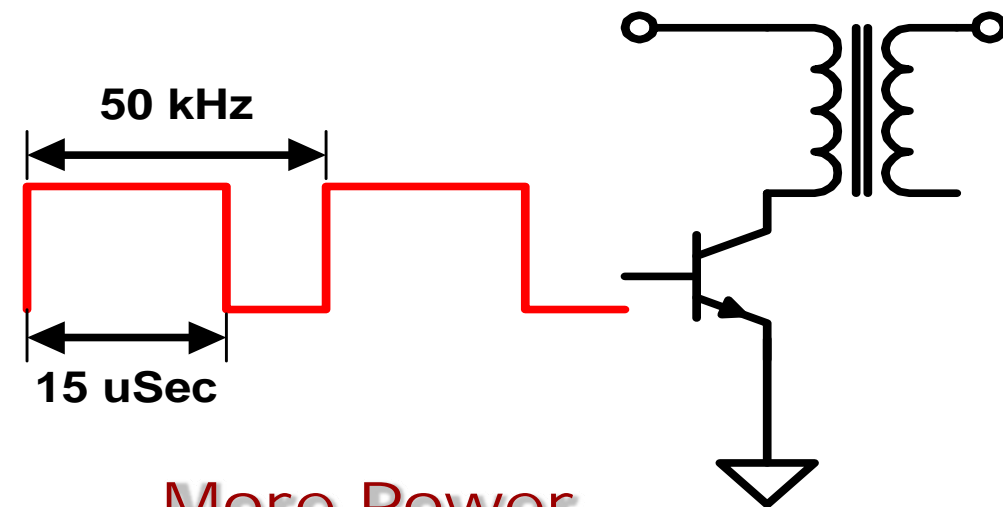


More Power

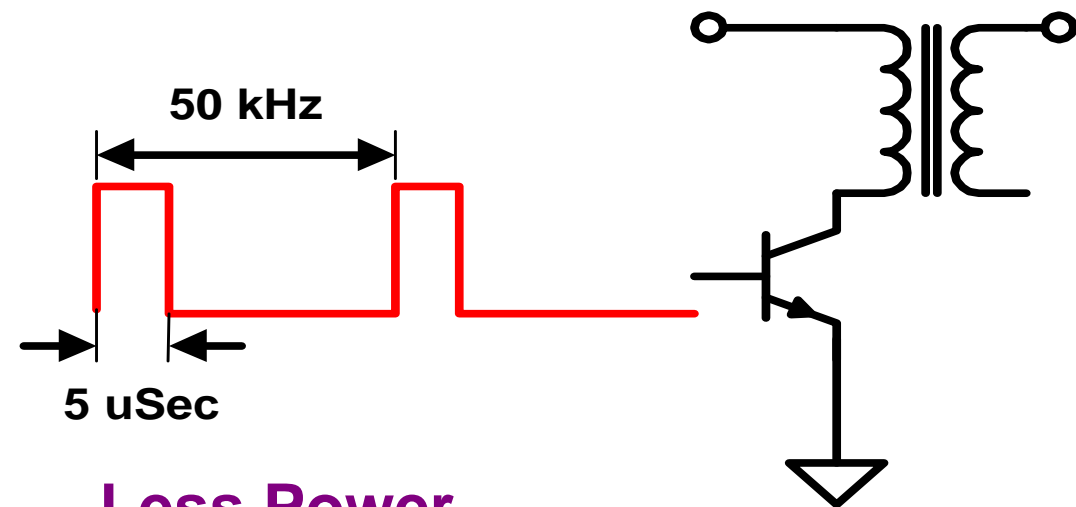


Less Power

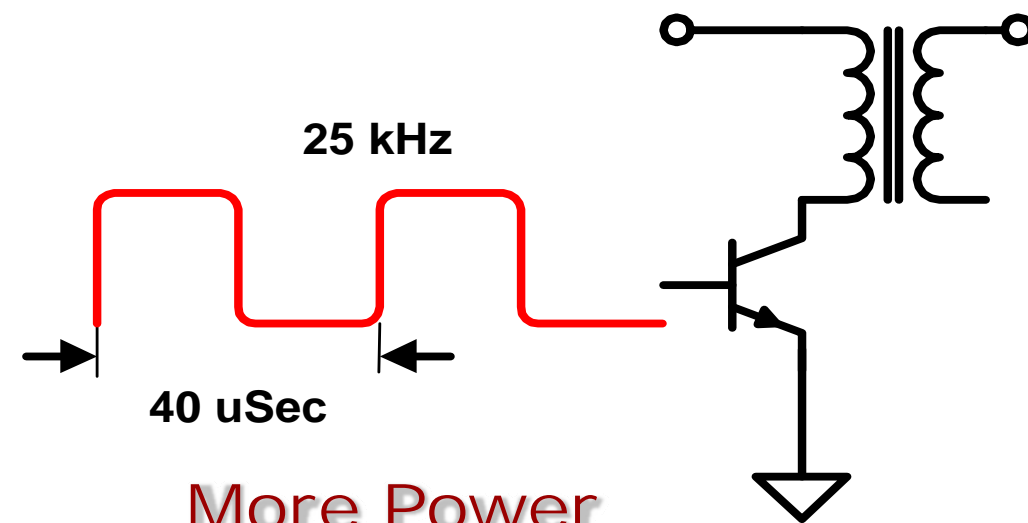Pulse Rate  $X_L = 2\pi fL > f \Rightarrow X_L = <$  power induced





More Power

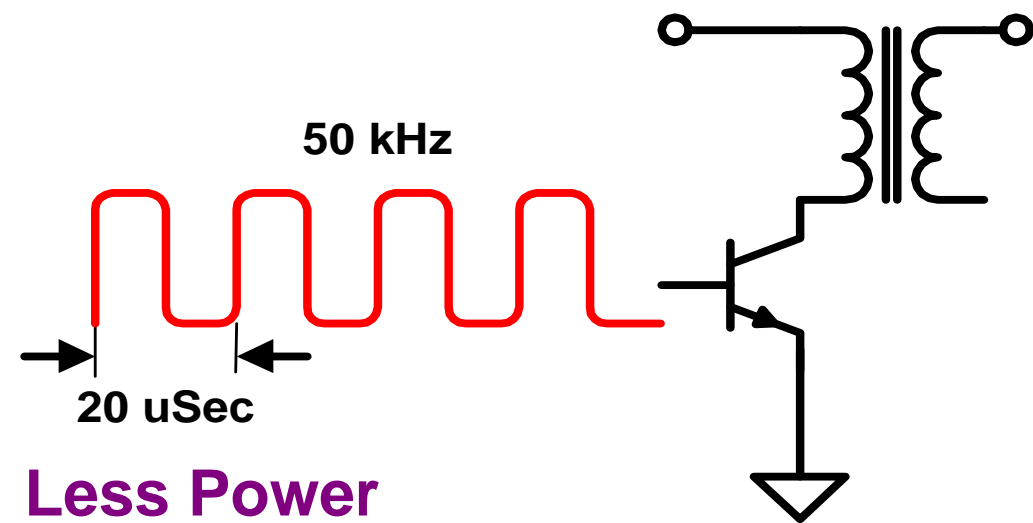


Less Power

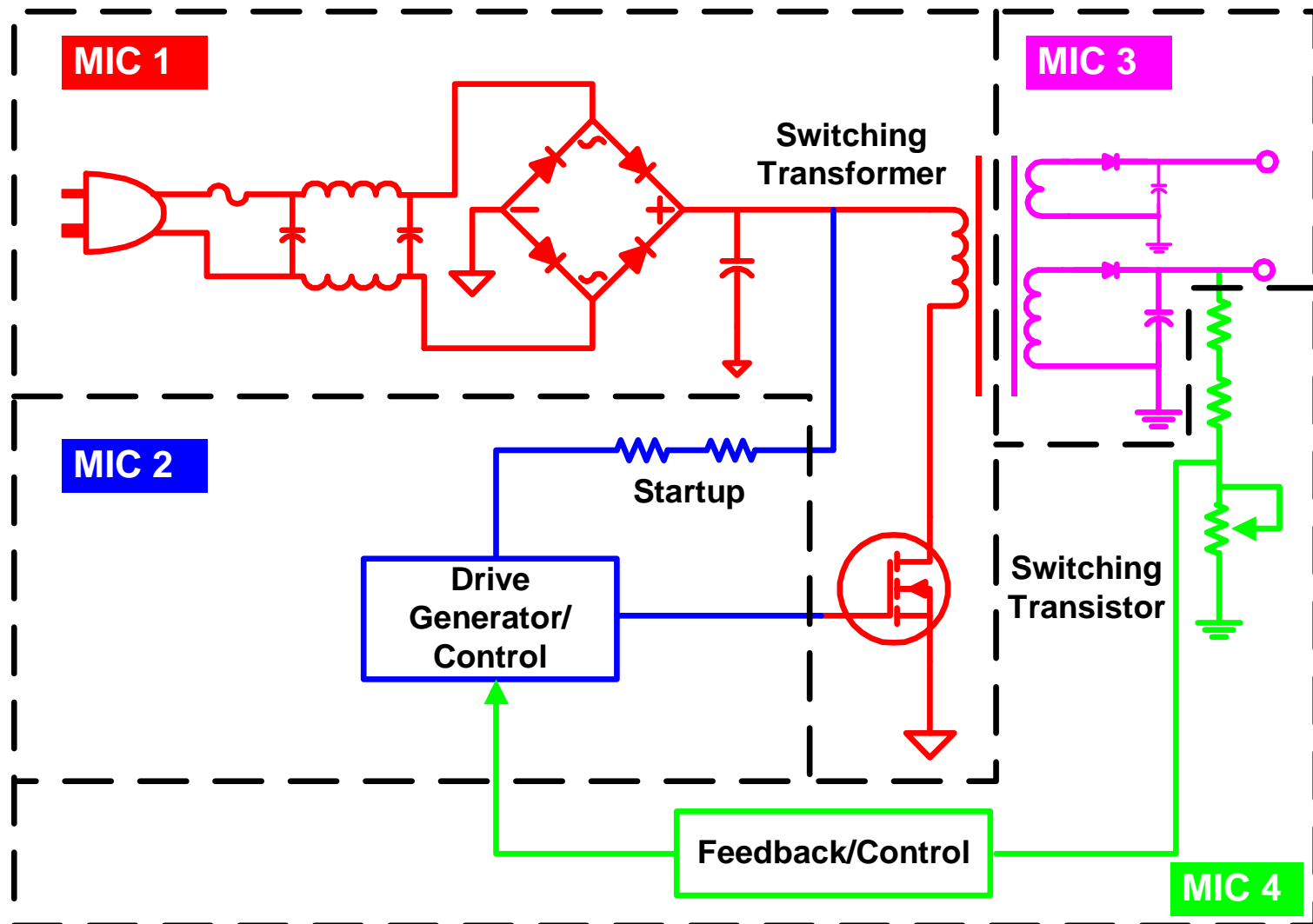- ◆ Simplified switch mode power supply block diagram with Most Important Circuits (MIC) identified





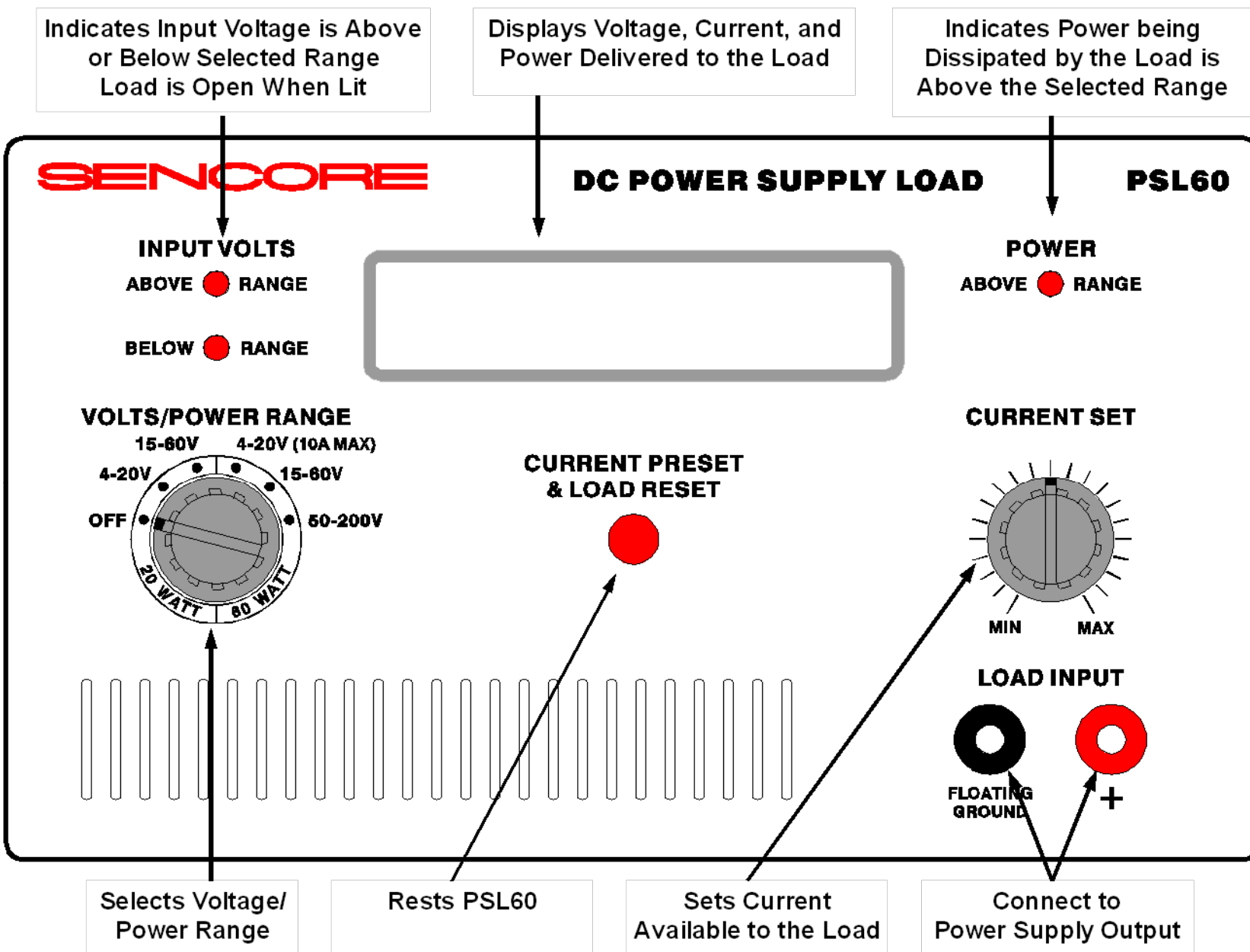

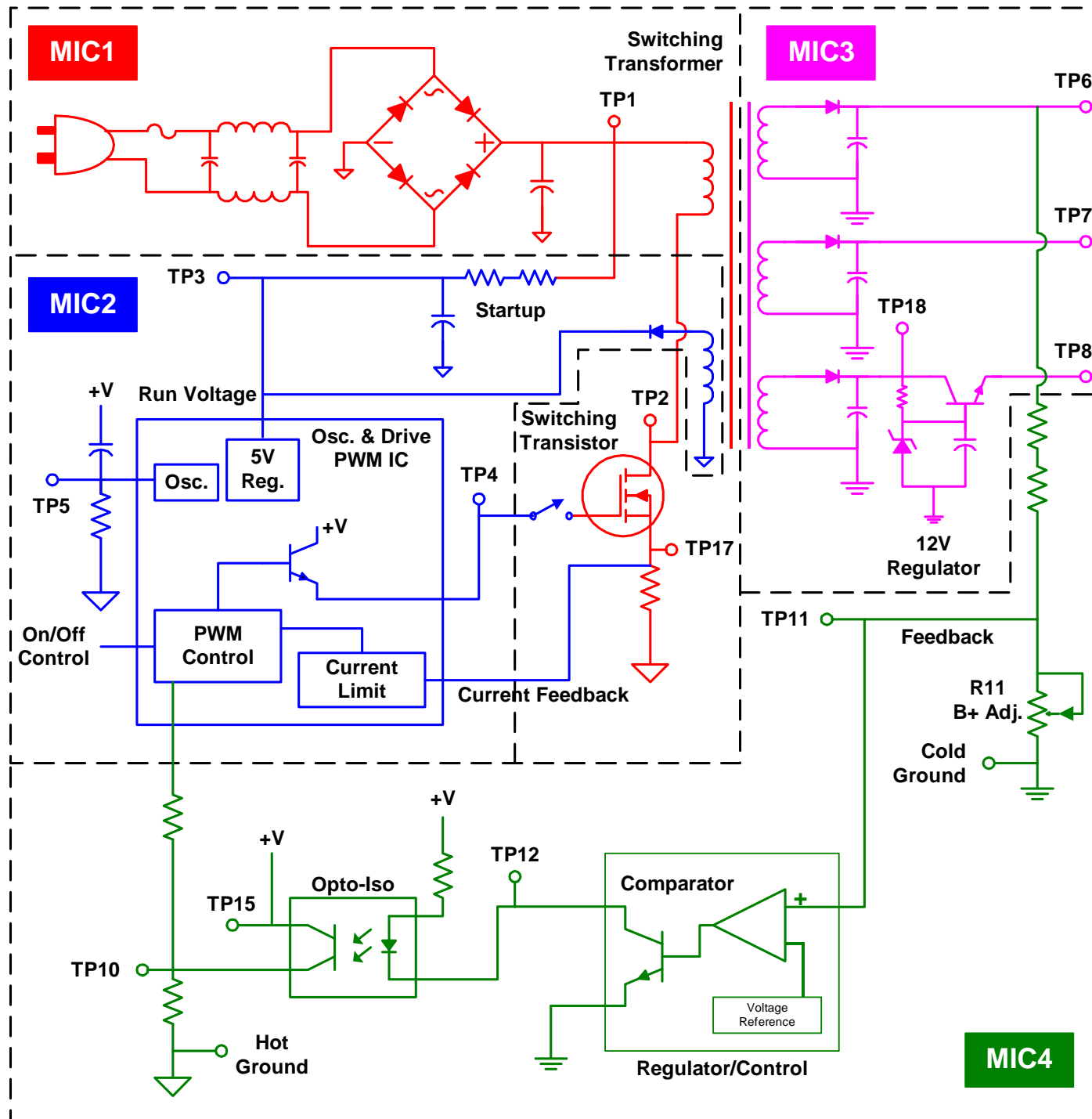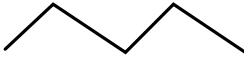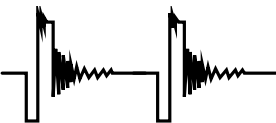
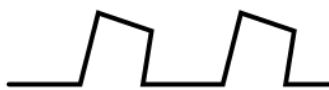






# Pulse Width SMPS

## Trainer Familiarization

<u>Test Point</u>	<u>Ground</u>	<u>DCV</u>	<u>VPP</u>	<u>Frequency</u>	<u>Timebase</u>	<u>Waveform</u>
TP1	HOT	157.3	5.3	120Hz	2ms	
TP2	HOT	157.3	331	25.5KHz	10μS	
TP3	HOT	15.3	N/A	None	None	None
TP4	HOT	2.0	14.7	25.5KHz	10μS	
TP5	HOT	1.9	1.76	25.5KHz	10μS	
TP10	HOT	2.28	.67	None	None	None
TP17	HOT	.06	2.5	25.5KHz	10μS	
TP6	COLD	150.0	.9	None	None	None
TP7	COLD	92.0	.7	None	None	None
TP8	COLD	12.5	.04	None	None	None
TP11	COLD	2.5	.158	None	None	None
TP12	COLD	9.28	.41	None	None	None



Pulse Width SMPS					Trainer Familiarization	
<u>Test Point</u>	<u>Ground</u>	<u>DCV</u>	<u>VPP</u>	<u>Frequency</u>	<u>Timebase</u>	<u>Waveform</u>
TP3	HOT	10 - 13	0 - 5.3	None	None	None
TP4	HOT	.5 - .9	1 - 6	None	5mS	
<u>AC Input Voltage</u>		<u>TP6 DCV</u>	<u>TP4 Total Time (1 cycle)</u>		<u>TP4 On Time (+ going)</u>	
40VAC		150	39.2μS		14μS	
120VAC		150	39.3μS		4μS	
<u>PSL5-50 Load Watts</u>	<u>Current PR570 Amps</u>	<u>Power PR570 Watts</u>	<u>TP6 DCV</u>	<u>TP4 Total Time 1 Cycle</u>	<u>TP4 On Time (+ going)</u>	<u>TP17 Delta DC</u>
10W	.17	23	150	39.2μS	4μS	.49
20W	.25	33	150	39.2μS	5μS	.60
30W	.31	40	150	39.2μS	6μS	.72
40W	.41	52	150	39.2μS	7μS	.84
50W	.48	65	149.2	39.2μS	8μS	.97

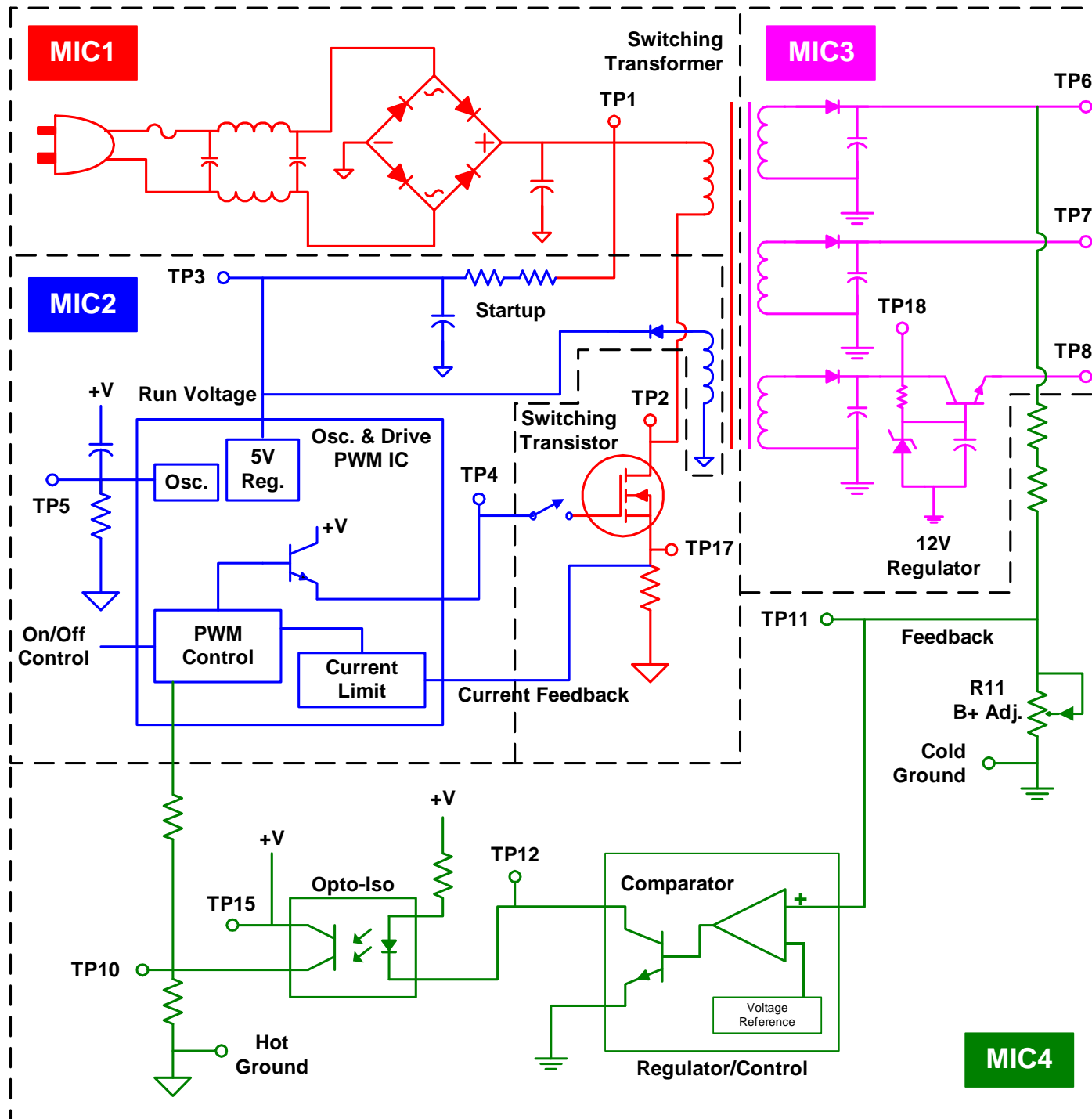

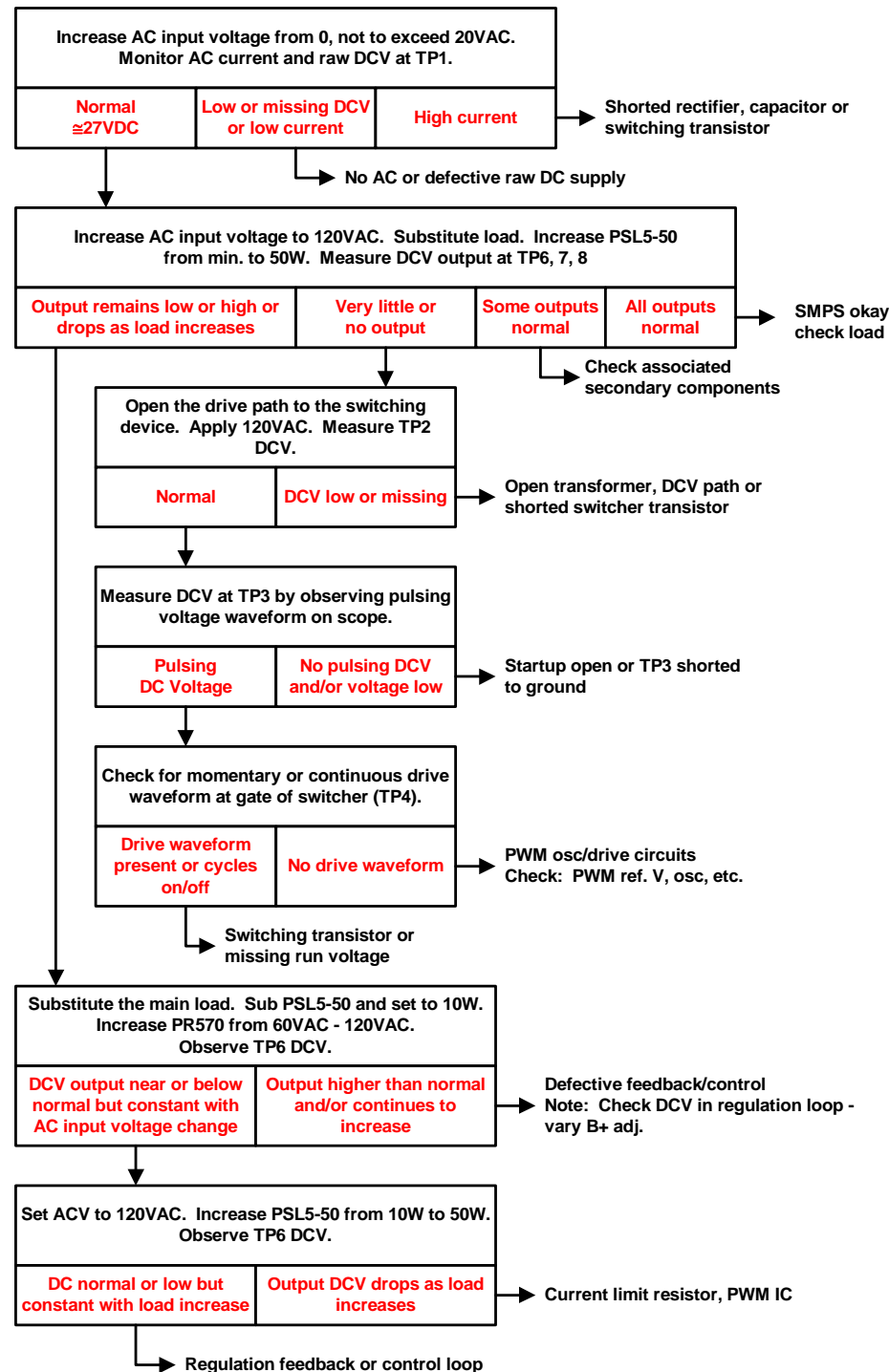


- ☑ **Check Raw DC Supply**
- ☑ **Check Regulated Outputs**
- ☑ **Check Primary DCV**
- ☑ **Check Startup**
- ☑ **Check PWM Osc/Drive**
- ☑ **Check Regulation/Feedback Control**
- ☑ **Check Current Control**

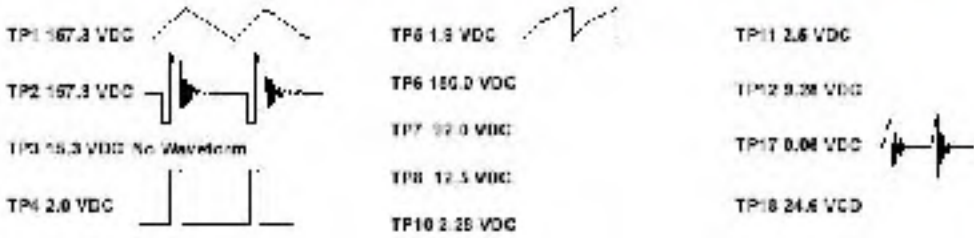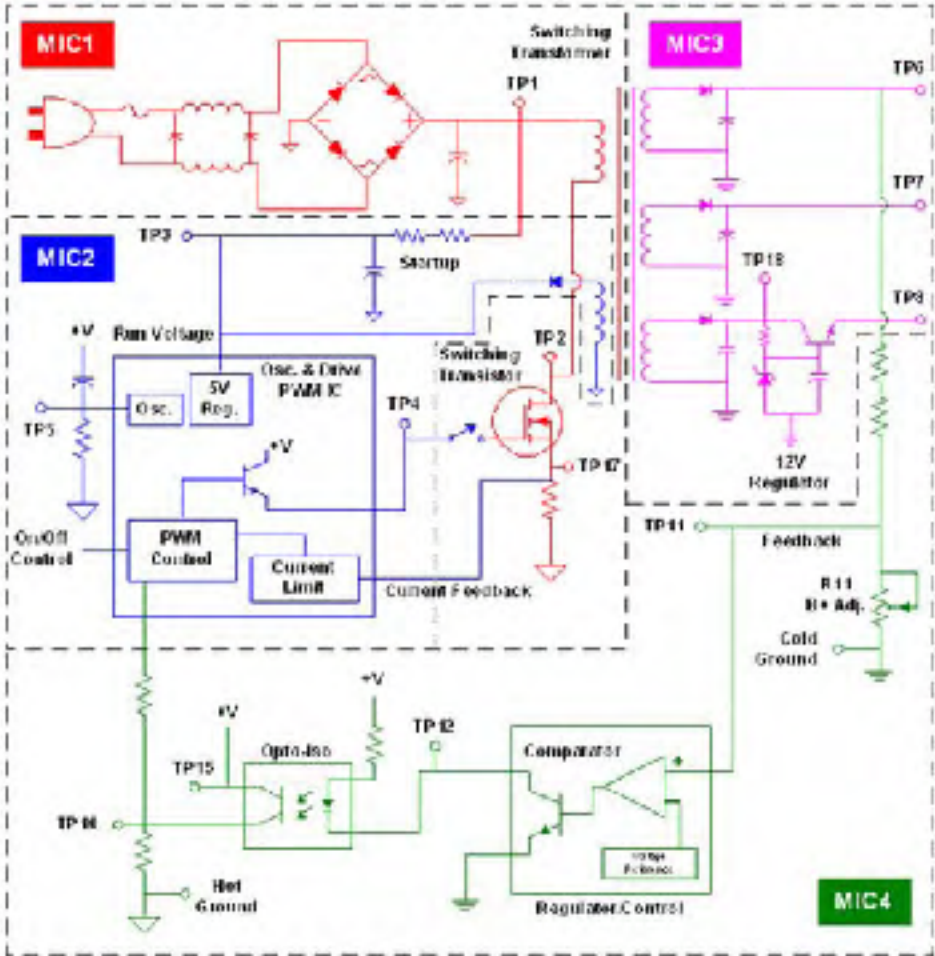Simplified Pulse Width Modulated (PWM) SMPS



Troubleshooting Tree

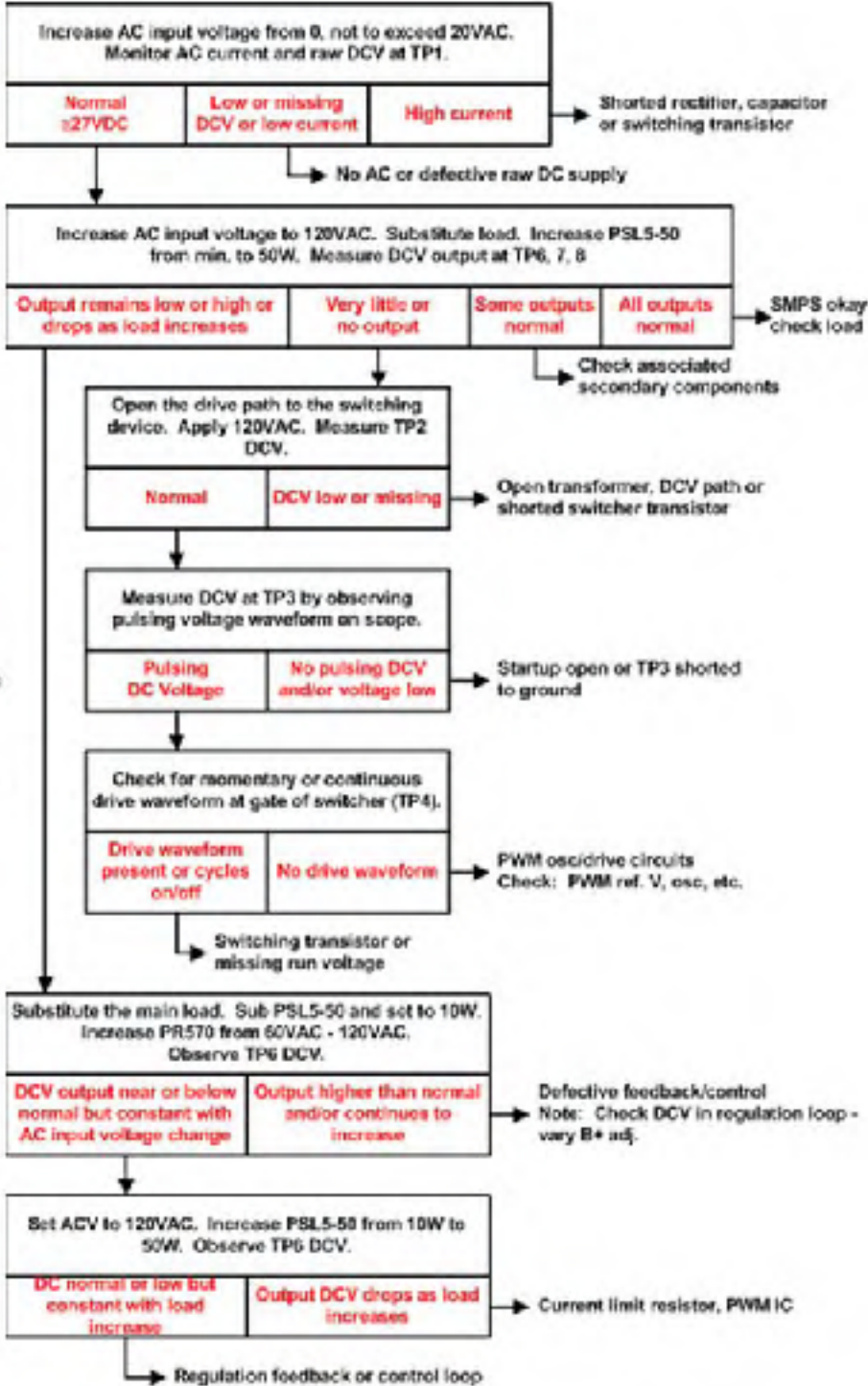


- ☑ **Check Raw DC Supply**
- ☑ **Check Regulated Outputs**
- ☑ **Check Primary DCV**
- ☑ **Check Startup**
- ☑ **Check PWM Osc/Drive**
- ☑ **Check Regulation/Feedback Control**
- ☑ **Check Current Control**

# Simplified Schematic



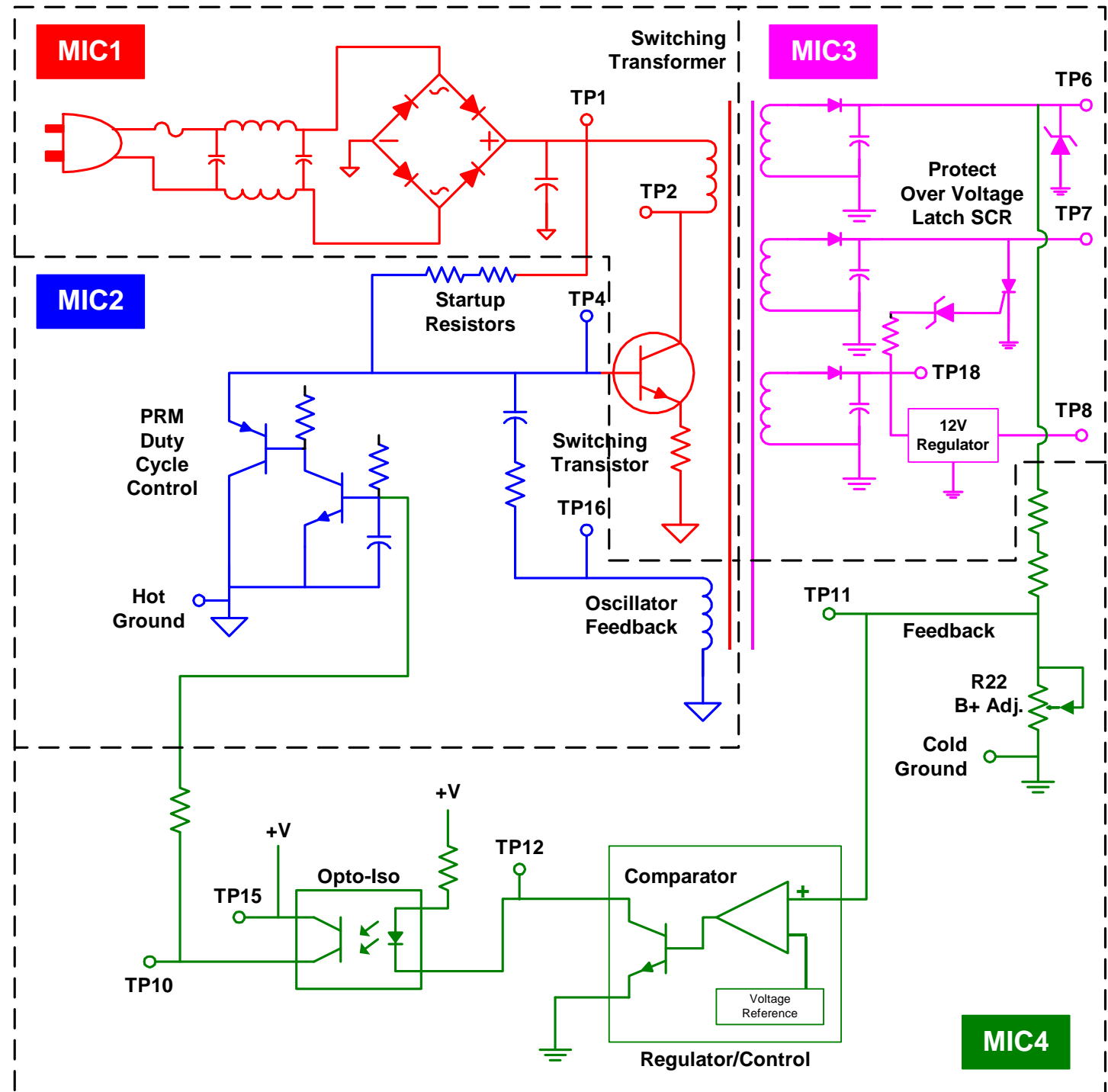

## Pulse Rate SMPS









- Able to self-protect
- “Crowbar shutdown



# Pulse Rate SMPS


## Trainer Familiarization

<u>Test Point</u>	<u>Ground</u>	<u>DCV</u>	<u>VPP</u>	<u>Frequency</u>	<u>Timebase</u>	<u>Waveform</u>
TP1	HOT	160	3.8	120Hz	2ms	
TP2	HOT	160	291	53KHz	5μS	
TP4	HOT	-.07	4	53KHz	5μS	
TP10	HOT	-.42	3.3	None	None	None
TP15	HOT	3.86	.35	None	None	None
TP16	HOT	0	12.6	53KHz	5μS	
TP6	COLD	180	.16	None	None	None
TP7	COLD	71.4	.07	None	None	None
TP8	COLD	12	.01	None	None	None
TP11	COLD	2.5	.08	None	None	None
TP12	COLD	8.95	.46	None	None	None
TP18	COLD	14.9	.06	None	None	None

Pulse Rate SMPS					Trainer Familiarization
<u>Test Point</u>	<u>Ground</u>	<u>VPP</u>	<u>Frequency</u>	<u>Timebase</u>	<u>Waveform</u>
TP4	HOT	1 - 3	≅ 40KHz	5μS	
<u>AC Input Voltage</u>		<u>TP6 DCV</u>	<u>TP4 Frequency</u>	<u>TP4 Waveform</u>	
40VAC		180	28KHz		
120VAC		180	77KHz		
<u>PSL5-50 Load Watts</u>	<u>Current PR570 Amps</u>	<u>Power PR570 Watts</u>	<u>TP6 DCV</u>	<u>TP4 Frequency</u>	<u>TP4 Waveform</u>
10W	.15	20	180	77KHz	
20W	.30	36	180	68KHz	
30W	.38	45	180	56KHz	
40W	.52	62	180	43KHz	
50W	.60	70	180	33KHz	

# Troubleshooting Tree

## Pulse Rate SMPS

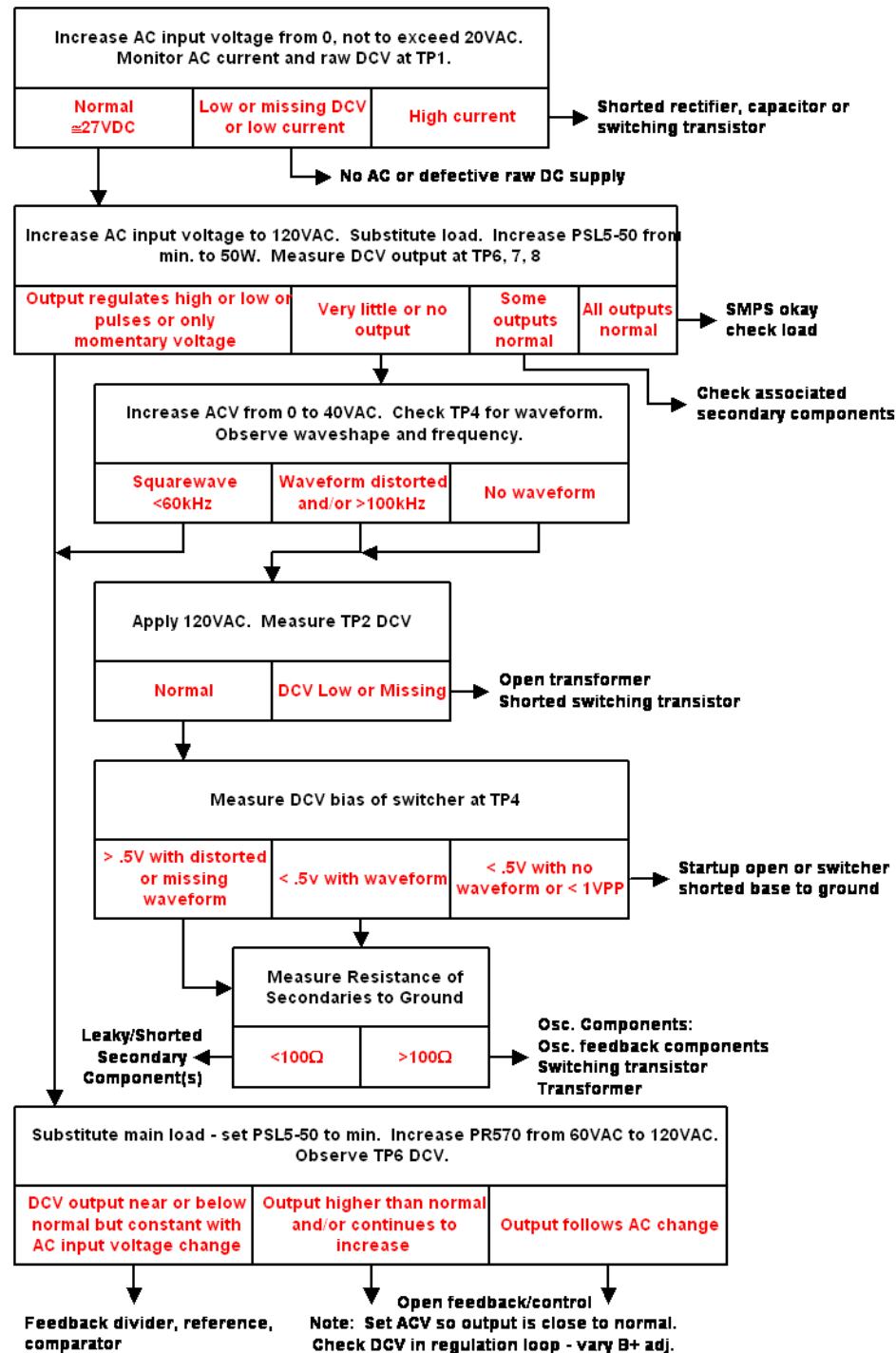

- ✓ **Check Raw DC Supply**
- ✓ **Check Regulated DC Outputs**
- ✓ **Check Self-Oscillation (waveshape/freq.)**
- ✓ **Check Primary DCV**
- ✓ **Check Startup**
- ✓ **Check Regulation/Feedback Control**

- ◆ **Once a defect has been localized, the suspect components should be tested**
  - ◆ **Only components that test bad should be replaced**
- ◆ **Random component replacement greatly increases the potential for error**
- ◆ **Many SMPS circuits are unforgiving**
  - ◆ **Component replacement errors may damage other components or create a second symptom or problem that may remain hidden, further complicating an already difficult repair**
- ◆ **SMPS circuits are less tolerant of components that age and change parameters**

## Capacitors fail in one of four ways


- ☞ Value Change
- ☞ Excessive dielectric absorption (DA)
- ☞ Excessive leakage
- ☞ High equivalent series resistance (ESR)



Value Change



ESR

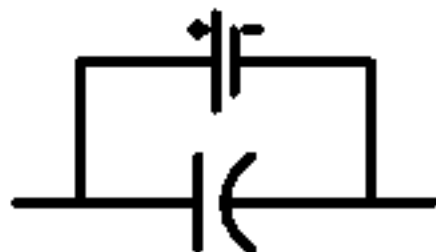


Dielectric Absorption



Leakage

*A value change alone is rare*

## What causes ESR

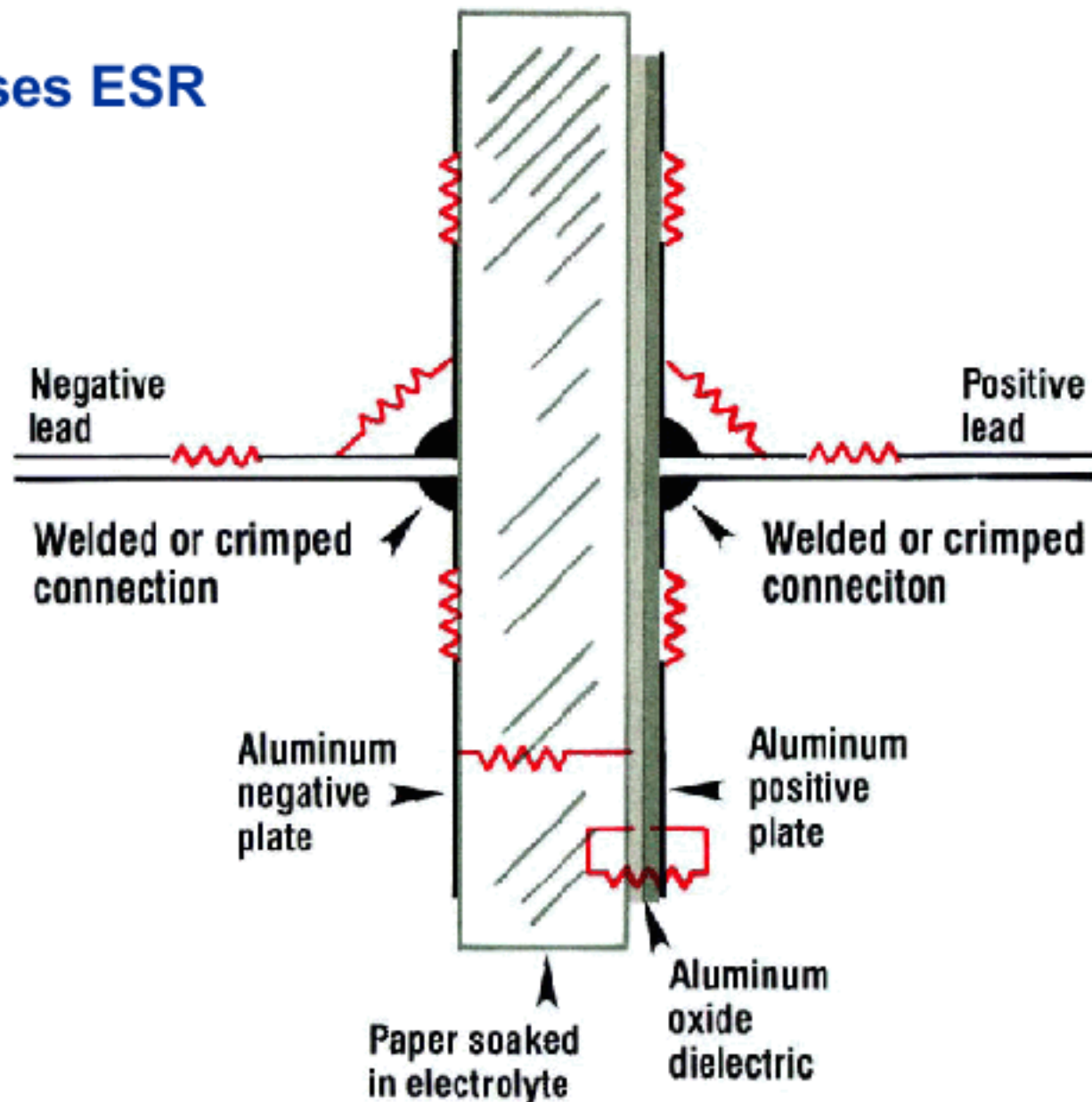


### Inductors and transformers fail in one of four ways

Open

Short

Value change

Shorted turn

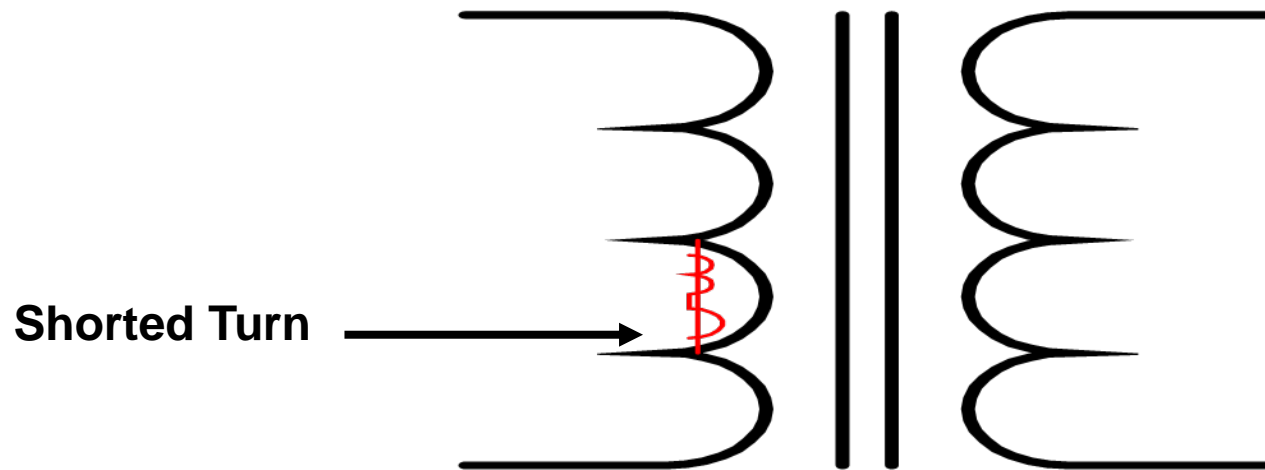

**The most common inductor and transformer failure is a single shorted turn within a winding**

**Transistors and diodes can fail in many ways**


**Short**

**Open**

**Leaky**

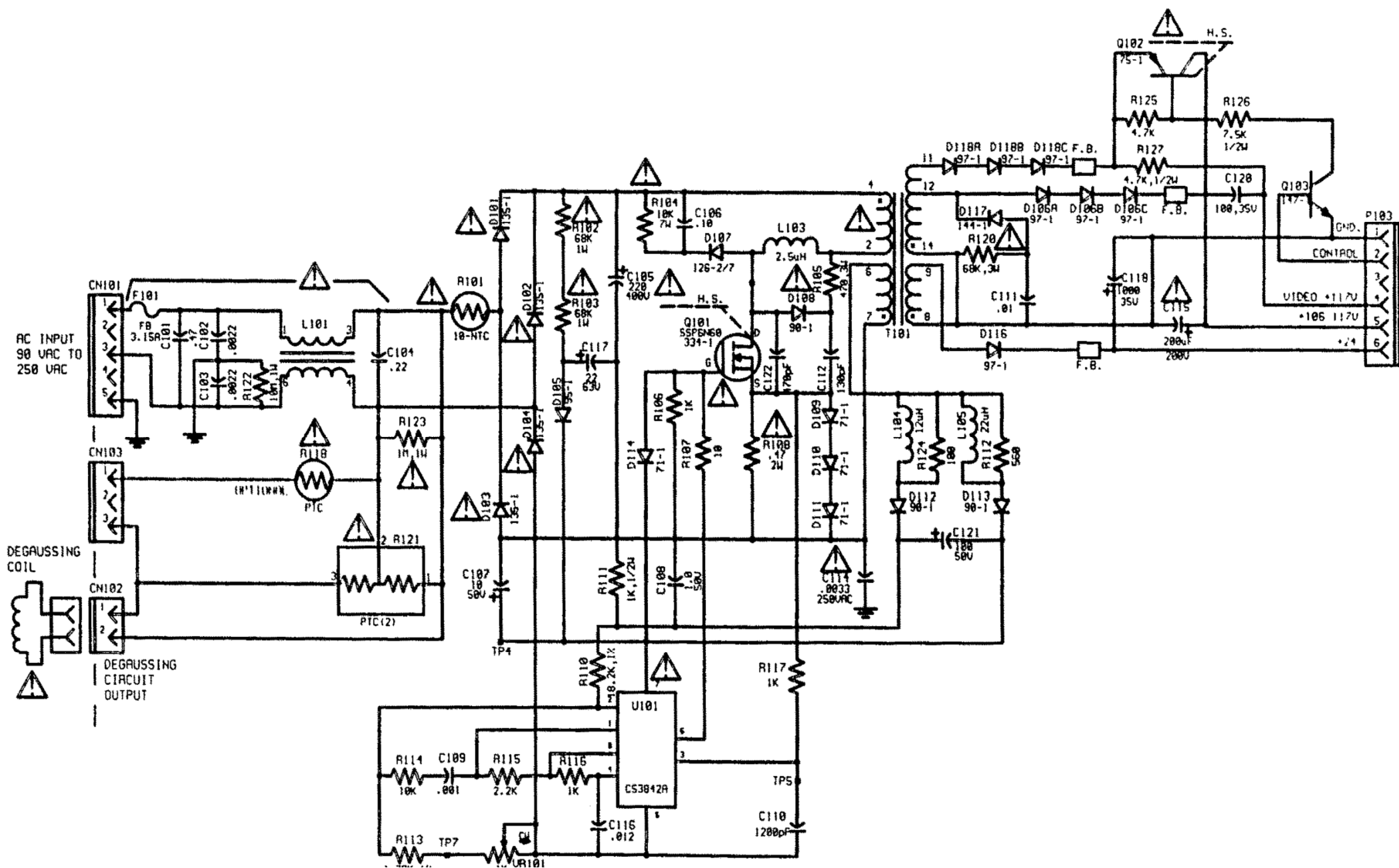
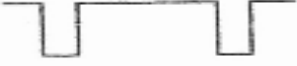








**Insufficient gain (beta)**

**Efficient SMPS troubleshooting requires the use of a thorough method to analyze components**




# SENCORE

## 10 Key Computer Monitor Waveforms

Waveform	Located At Block Diagram Test Points	Waveform	Located At Block Diagram Test Points
<b>1</b>  Raster Pattern Waveform	R,G,B Video 11, 12, 13, 14, 21, 22, 23, 24, 31, 32, 33, 34	<b>6</b> 	Horizontal Sync Buffer Input, Output, 50
Vert Atten : 1 VPP to 10 VPP Waveform Analyzer Setting: Timebase : 5 $\mu$ sec Horiz. (VGA) : 10 msec Vert.		Waveform Analyzer Setting: Vert Atten: 1 VPP Timebase: 5 $\mu$ sec	
<b>2</b> 	Vertical Sync. Buffer Input, Output, 40	<b>7</b> 	Horizontal Osc. 51
Waveform Analyzer Setting: Vert Atten: 1 VPP Timebase: 10 msec		Waveform Analyzer Setting: Vert Atten: 2 VPP (VGA) Timebase: 5 $\mu$ sec	
<b>3</b> 	Vertical Oscillator 41	<b>8</b> 	Horizontal Driver Output Collector * 52
Waveform Analyzer Setting: Vert Atten: 1 VPP Timebase: 10 msec		Waveform Analyzer Setting: Vert Atten: 50 VPP Timebase: 5 $\mu$ sec	
<b>4</b> 	Vertical Driver Output 42	<b>9</b> 	Horizontal Output Base Drive * 52
Waveform Analyzer Setting: Vert Atten: 1 VPP Timebase: 10 msec		Waveform Analyzer Setting: Vert Atten: 5 VPP Timebase: 5 $\mu$ sec	
<b>5</b> 	Vertical Output 43	<b>10</b> 	Horizontal Output Collector ** 50
Waveform Analyzer Setting: Vert Atten: 20 VPP Timebase: 10 msec		Waveform Analyzer Setting: Vert Atten: 200 VPP Timebase: 5 $\mu$ sec	

\* One test point location with two waveforms represents voltage output waveform transformed to a current input waveform.  
 \*\* \*Caution\* - Most oscilloscopes can be damaged attempting to measure this waveform
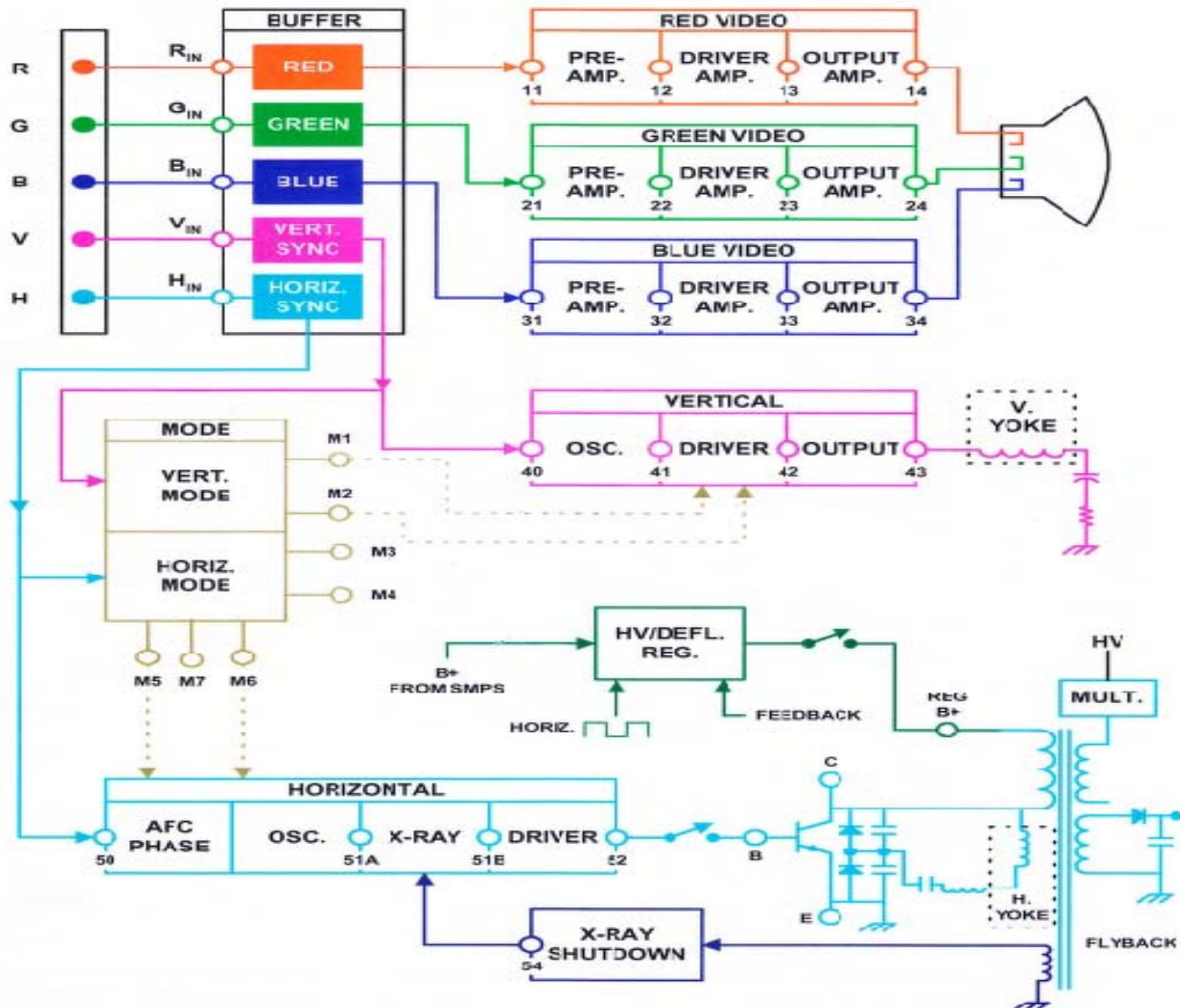
# Universal Computer Monitor      Block Diagram




[illegible]


The diagram illustrates the electrical connections for an LCD driver circuit. It includes the following components and their interconnections:

- Top Back light Assembly 2 or 3 CCFLs:** Connected to the Timing Controller & LVDS Receiver and the Source Driver Circuit. It includes a ground return (Gnd. Rtn.) and a 1, 2 IN connection.
- Timing Controller & LVDS Receiver:** Receives LVDS #1 and LVDS #2 signals. It is connected to the Gate Driver Circuit, the Power Circuit Block, and the Source Driver Circuit. It also provides RGB signals to the Source Driver Circuit.
- Gate Driver Circuit:** Connected to the Timing Controller & LVDS Receiver and the TFT-LCD Panel (G1 and G1024).
- TFT-LCD Panel 1280 X RGB X 1024 Pixels:** Receives signals from the Gate Driver Circuit (G1, G1024) and the Source Driver Circuit (S1, S1280).
- Power Circuit Block:** Receives PNL and VCC signals. It is connected to the Timing Controller & LVDS Receiver and the Source Driver Circuit.
- Source Driver Circuit:** Receives signals from the Timing Controller & LVDS Receiver, the Power Circuit Block, and the Gate Driver Circuit. It provides signals to the TFT-LCD Panel and the Bottom Back light Assembly.
- Bottom Back light Assembly 2 or 3 CCFLs:** Connected to the Source Driver Circuit. It includes a ground return (Gnd. Rtn.).

3, 4  
Input

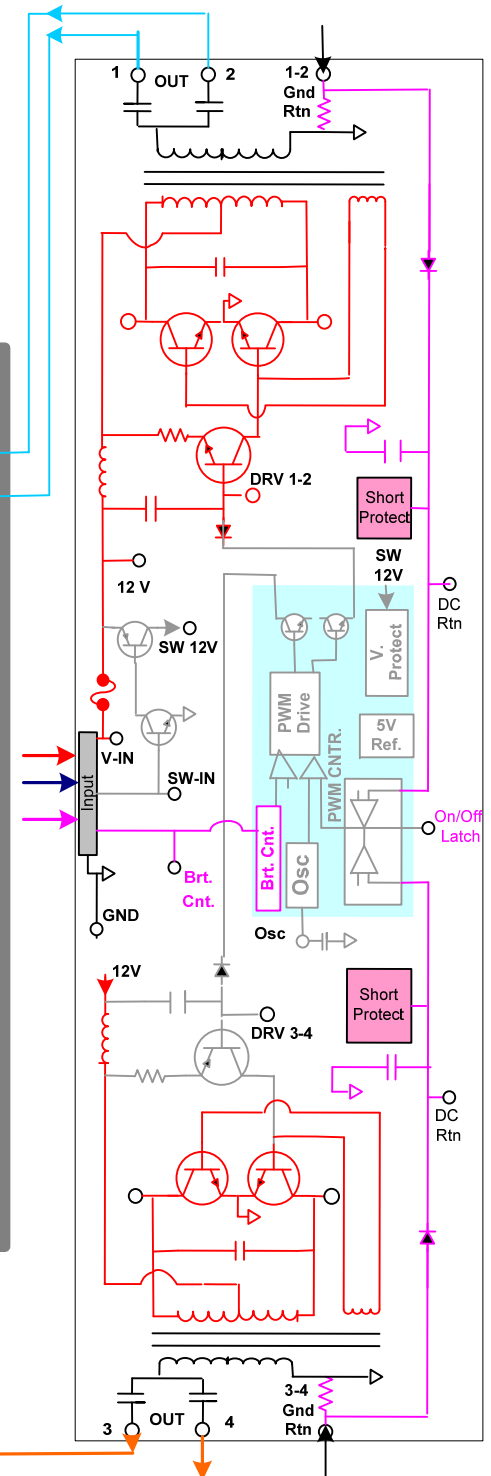
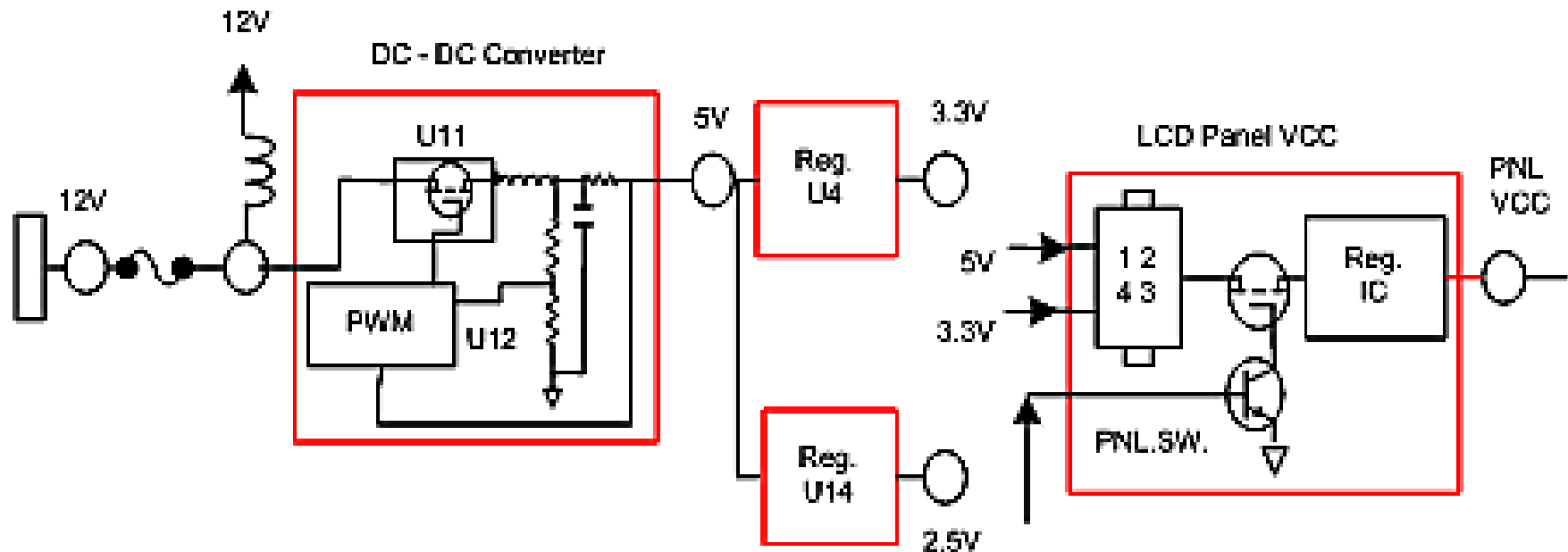
# Main Signal Processing/Controller Board Power Supplies




The main signal processing/controller board typically requires 3 power supply voltages - 5V, 3.3V, and 2.5V power supply.

A DC-to-DC converter is a switching power supply that bucks the input 12V down to 5V. The converter outputs a stable regulated 5V

The 5V output feeds linear regulator ICs to drop voltages down to 3.3V and 2.5V outputs. The 3.3V and 2.5V DC supplies are conventional fixed voltage regulators.

A Panel VCC supply selects (mechanical jumper) an input voltage and the microprocessor switches it (on/off) to the LCD panel.
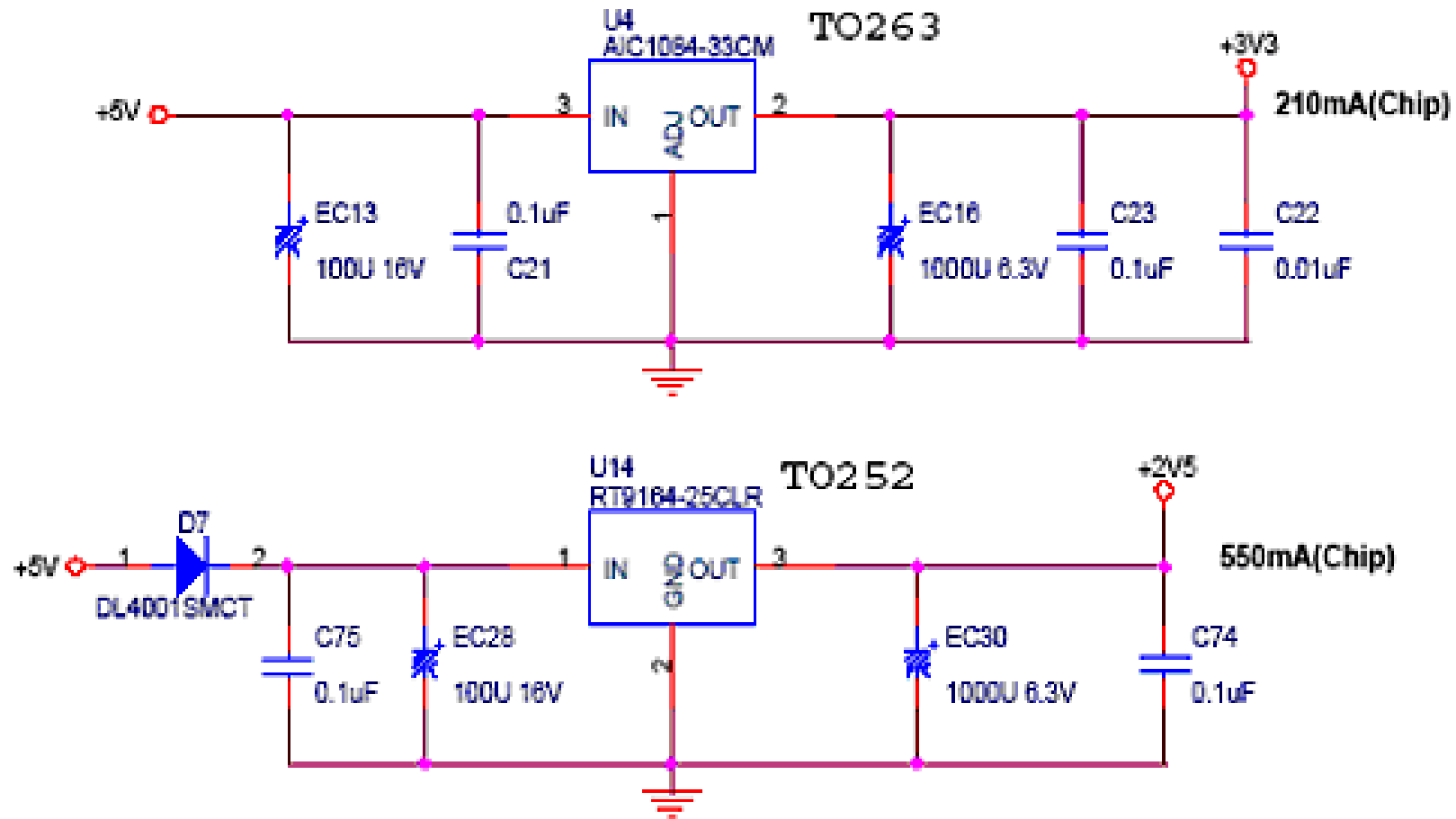
# Main Signal Processing/Controller Board Power Supplies



The 3.3V and 2.5V power supplies operate the digital ICs on the signal processor/controller circuit board. These supply voltages are derived from the 5V power supply. U14 is a surface mount linear regulator IC that outputs a regulated 2.5V. It is an IC package TO-252 and a suitable replacement is a PJ1117CP-2.5. U4 is also a linear regulator but physically larger.

A suitable replacement is PJ1084CM.

PNL VCC (FL1)

TXCK+E (CN1 pin 3)

3.3 Volts +  
(U4 heatsink)

040914240  
AP72505-1A

ACTE  
G18  
LB

XTAL (C44)

TCLK (C45)

5 Volts + (R23)

Horiz. Out  
(U13, pin 10)

12 Volts + (F1)

Vert. Out  
(U13, pin 8)

Horiz. In (R49)

Vert In (R57)

Blue In (R58)

Red In (R60)


2.5 Volt + (U14 heatsink)


SDA (ZD2)

SCL (ZD1)

Green In (R59)

Reset (R29)

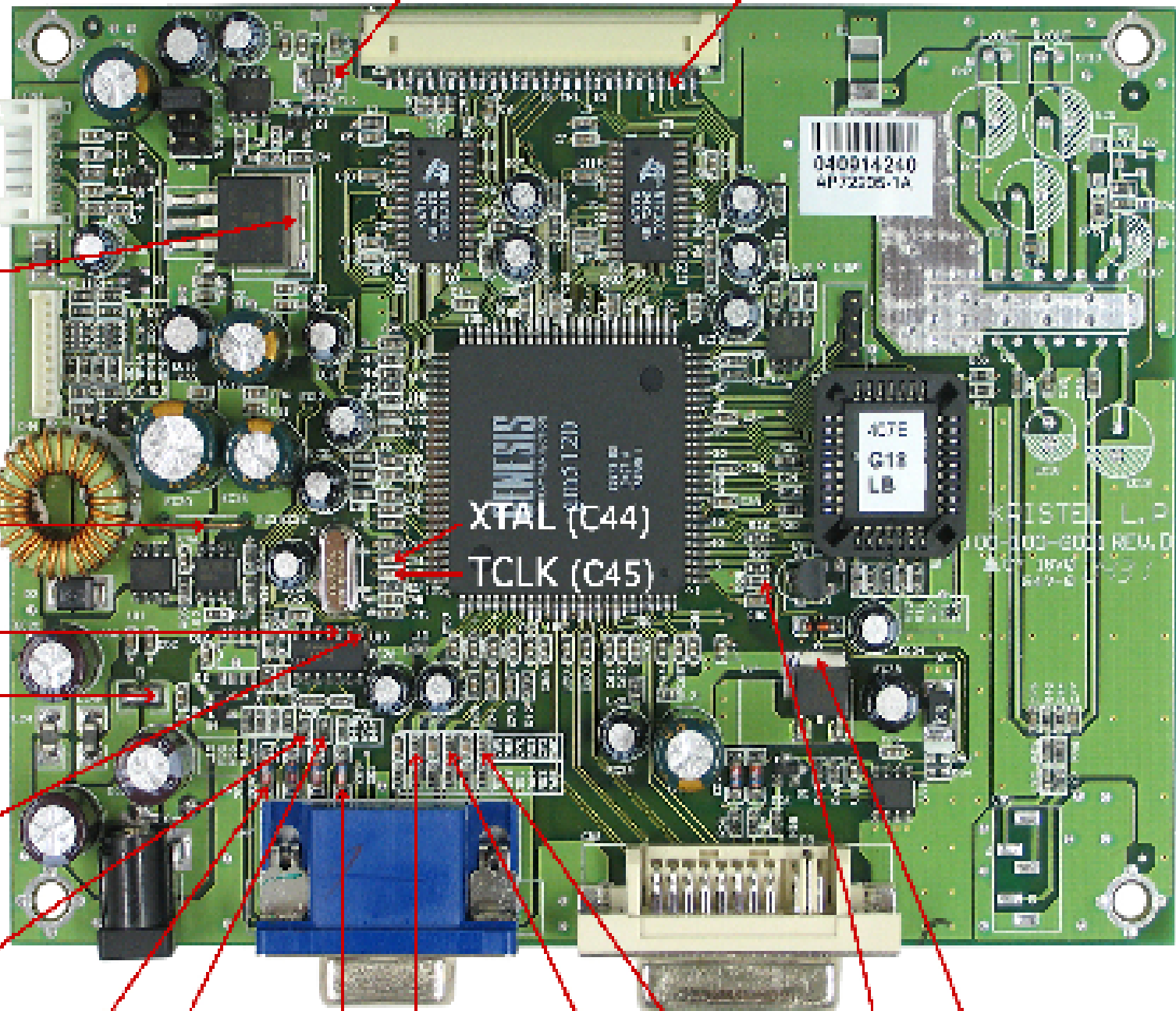

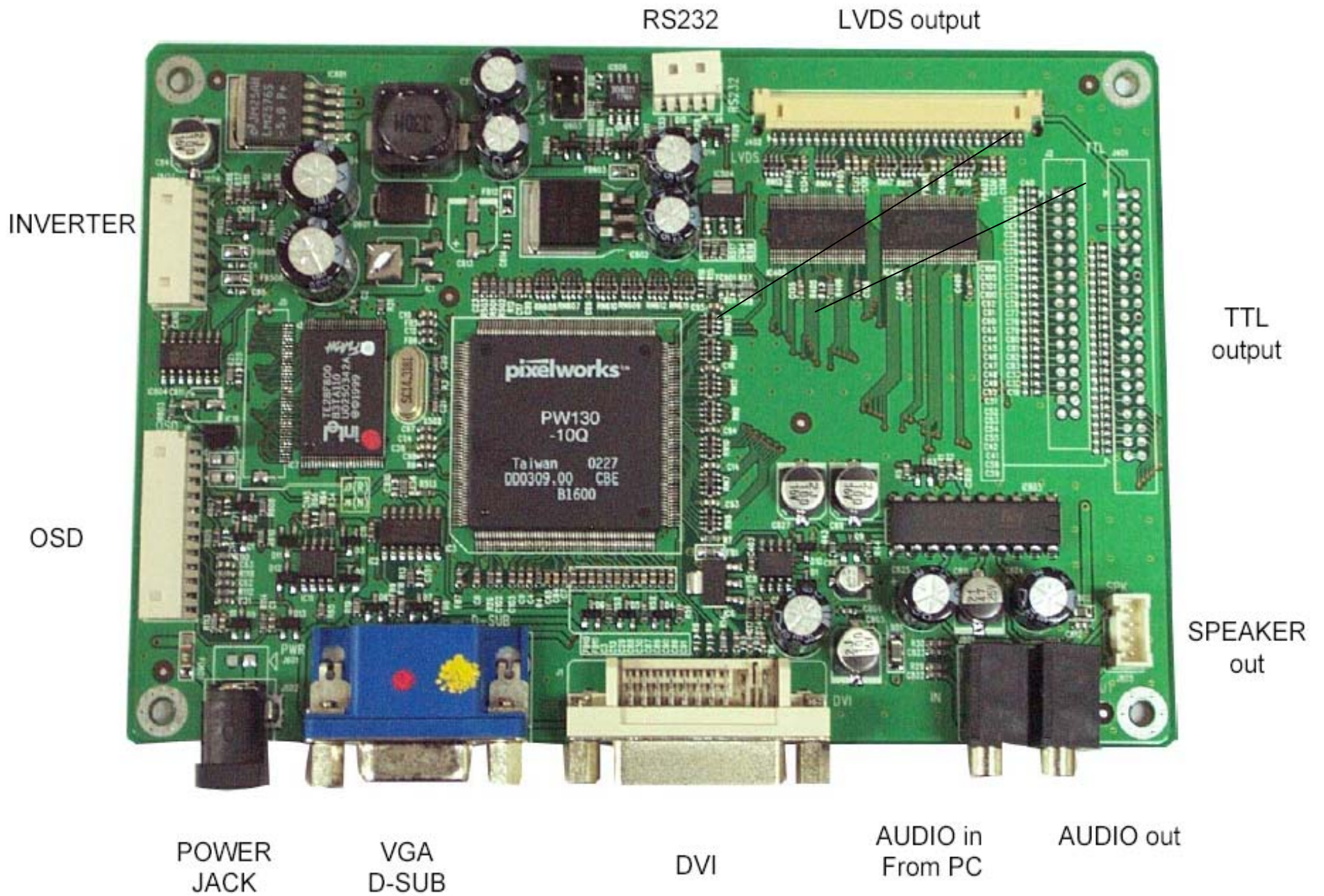


Signal processor/controller circuit board. (Courtesy Ceronix)

# Welcome

## *Amusement & Music Operators Association*
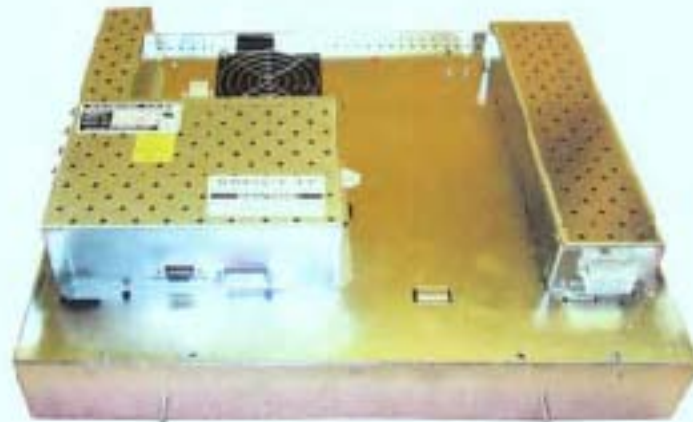
### **LCD Power Supply Troubleshooting Tech Seminar**



**INSTRUCTOR: Ray Holdren,**  
*Kokopelli Consulting LAS Vegas*  
*Instructor for CSN's Workforce Development Group*  
*Teacher for College of Southern Nevada, Cheyenne Campus, North Las Vegas, NV*

*Ray.Holdren@csn.edu*